



HY313X

Configurations

Table of Contents

1. DCMV	6
1.1. Input Network Configuration.....	6
1.2. DC50mV Measurement Network Configuration.....	7
1.3. DC500mV Measurement Network Configuration.....	8
2. ACMV	9
2.1. Input Network Configuration.....	9
2.2. AC50mV Measurement Network Configuration.....	10
2.3. AC500mV Measurement Network Configuration.....	11
3. DCV	12
3.1. 5V Input Network Configuration	12
3.2. 50V Input Network Configuration	13
3.3. 500V Input Network Configuration	14
3.4. 1000V Input Network Configuration	15
3.5. DC5V~1000V Measurement Network Configuration	16
4. ACV	17
4.1. 5V Input Network Configuration	18
4.2. 50V Input Network Configuration	19
4.3. 500V Input Network Configuration	20
4.4. 1000V Input Network Configuration	21
4.5. AC5V~1000V Measurement Network Configuration	22
5. CAPACITANCE	23


5.1.	50-500nF (Constant Voltage Charge/Discharge Measurement).....	24
5.2.	5uF-50uF (Constant Current Charge/Discharge Measurement)	25
5.3.	500uF(Charge).....	26
5.4.	5mF-50mF(Charge)	27
5.5.	500uF~50mF Measurement Network Configuration.....	28
5.6.	Discharge (500uF~50mF)	29
6.	RESISTOR	31
6.1.	50ohm/500ohm Input Network Configuration	33
6.2.	5K ohm Input Network Configuration	34
6.3.	50ohm Measurement Network Configuration	35
6.4.	500 ohm~50K ohm Measurement Network Configuration.....	36
6.5.	50Kohm Input Network Configuration	37
6.6.	500Kohm Input Network Configuration	38
6.7.	5M ohm Input Network Configuration	39
6.8.	50Mohm Input Network Configuration	40
6.9.	500Kohm~50Mohm Measurement Network Configuration.....	41
7.	DIODE	42
7.1.	Diode Input Network Configuration	42
7.2.	Diode Measurement Network Configuration	43
8.	CONTINUITY.....	44
9.	CURRENT	45
9.1.	DC 50mA.....	45
9.2.	DC 500mA.....	46

9.3.	AC 50mA	47
9.4.	AC 500mA	48
10.	FREQUENCY	49
10.1.	Frequency Counter Calculation Example Description	50
10.2.	Voltage input (Analog Input)	51
10.3.	Current input (Analog Input)	52
10.4.	CNT input (Digital Input)	53
11.	REVISION HISTORY	55


Attention :

1. HYCON Technology Corp. reserves the right to change the content of this datasheet without further notice. For most up-to-date information, please constantly visit our website:
<http://www.hycontek.com> .
2. HYCON Technology Corp. is not responsible for problems caused by figures or application circuits narrated herein whose related industrial properties belong to third parties.
3. Specifications of any HYCON Technology Corp. products detailed or contained herein stipulate the performance, characteristics, and functions of the specified products in the independent state. We does not guarantee of the performance, characteristics, and functions of the specified products as placed in the customer's products or equipment. Constant and sufficient verification and evaluation is highly advised.
4. Please note the operating conditions of input voltage, output voltage and load current and ensure the IC internal power consumption does not exceed that of package tolerance. HYCON Technology Corp. assumes no responsibility for equipment failures that resulted from using products at values that exceed, even momentarily, rated values listed in products specifications of HYCON products specified herein.
5. Notwithstanding this product has built-in ESD protection circuit, please do not exert excessive static electricity to protection circuit.
6. Products specified or contained herein cannot be employed in applications which require extremely high levels of reliability, such as device or equipment affecting the human body, health/medical equipments, security systems, or any apparatus installed in aircrafts and other vehicles.
7. Despite the fact that HYCON Technology Corp. endeavors to enhance product quality as well as reliability in every possible way, failure or malfunction of semiconductor products may happen. Hence, users are strongly recommended to comply with safety design including redundancy and fire-precaution equipments to prevent any accidents and fires that may follow.
8. Use of the information described herein for other purposes and/or reproduction or copying without the permission of HYCON Technology Corp. is strictly prohibited.

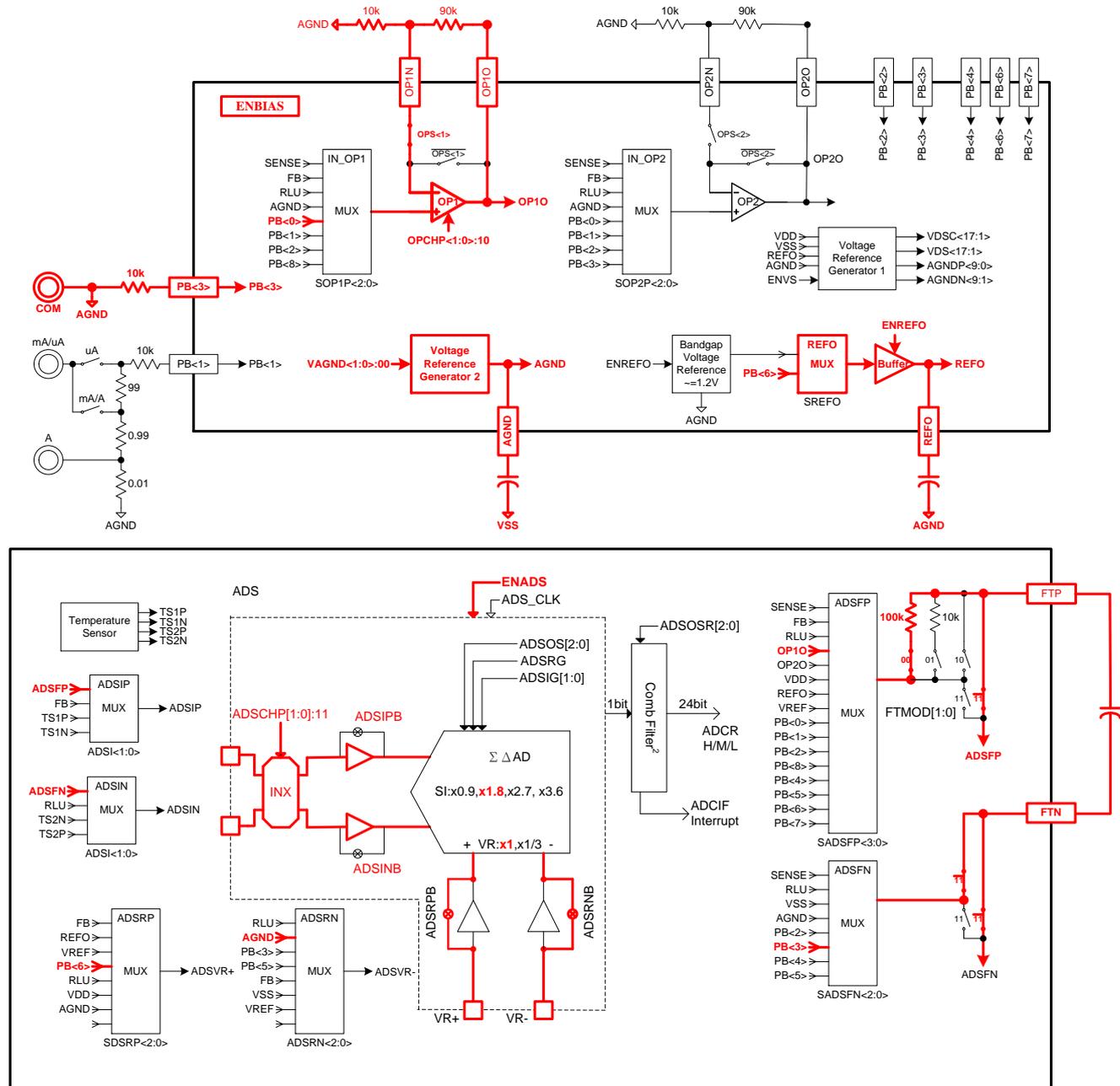1.2. DC50mV Measurement Network Configuration



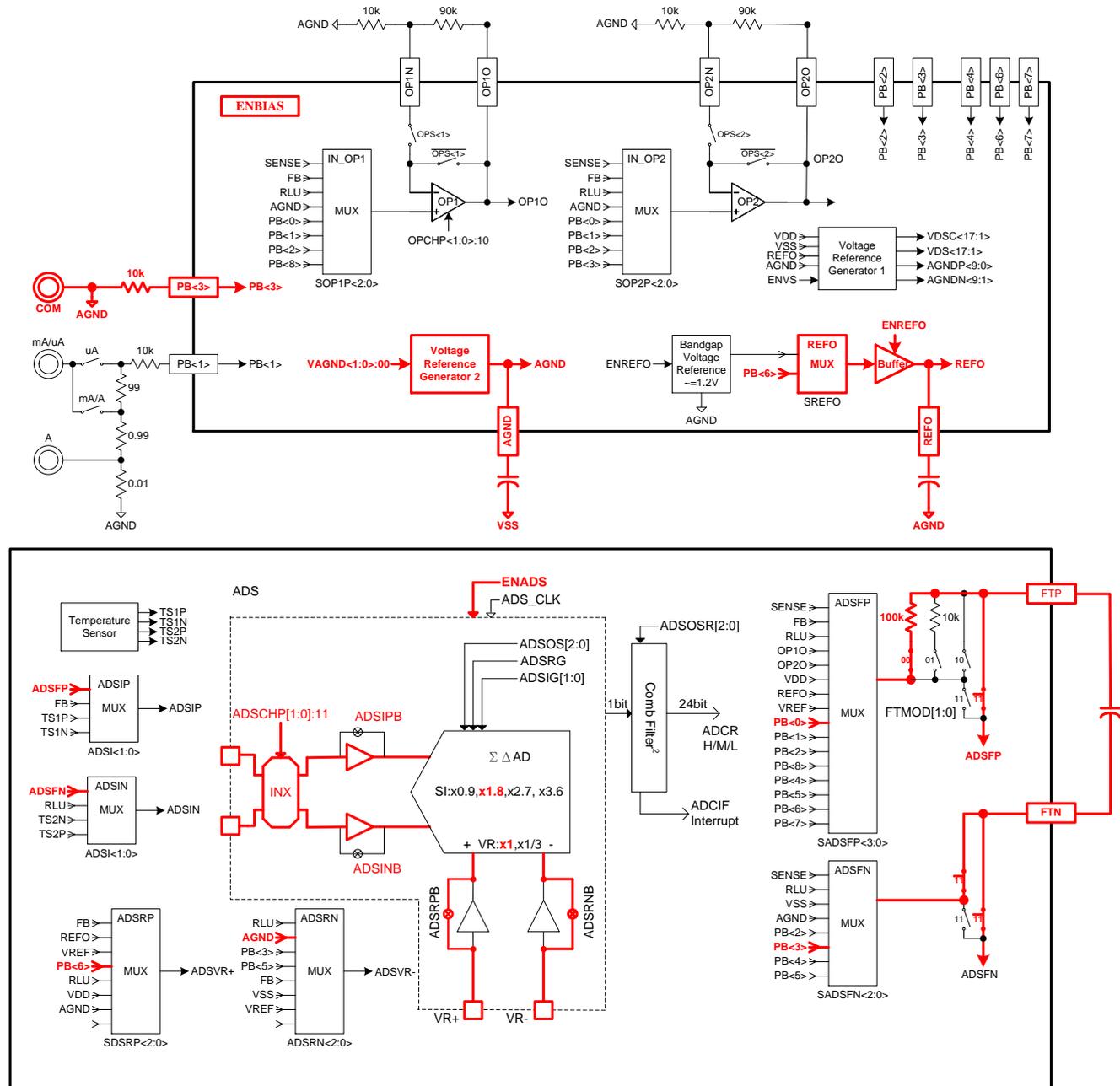1.3. DC500mV Measurement Network Configuration




2. ACmV


Due to high ADC input impedance, it is easily to sense 50/60Hz signal of the air that leads to unstable reading value after the testing probe was connected. It is recommended to connect input $10M\Omega$ to ground to reduce input impedance of DMM mV range.

The network configuration of 50mV and 500mV is similar. When measuring 50mV, it uses built-in OPA to amplify signal for 10 times then processing it in ADC.


2.1. Input Network Configuration

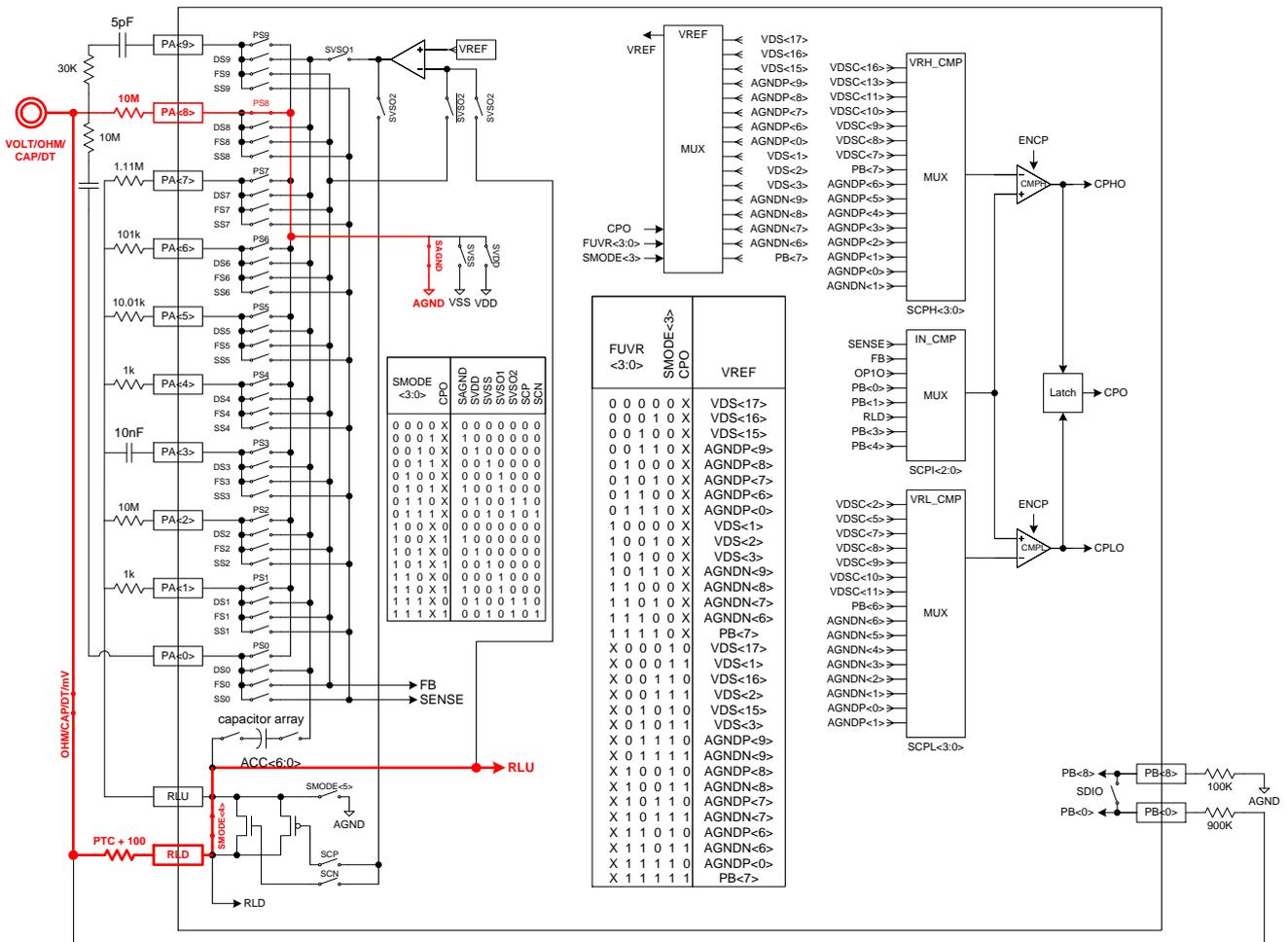

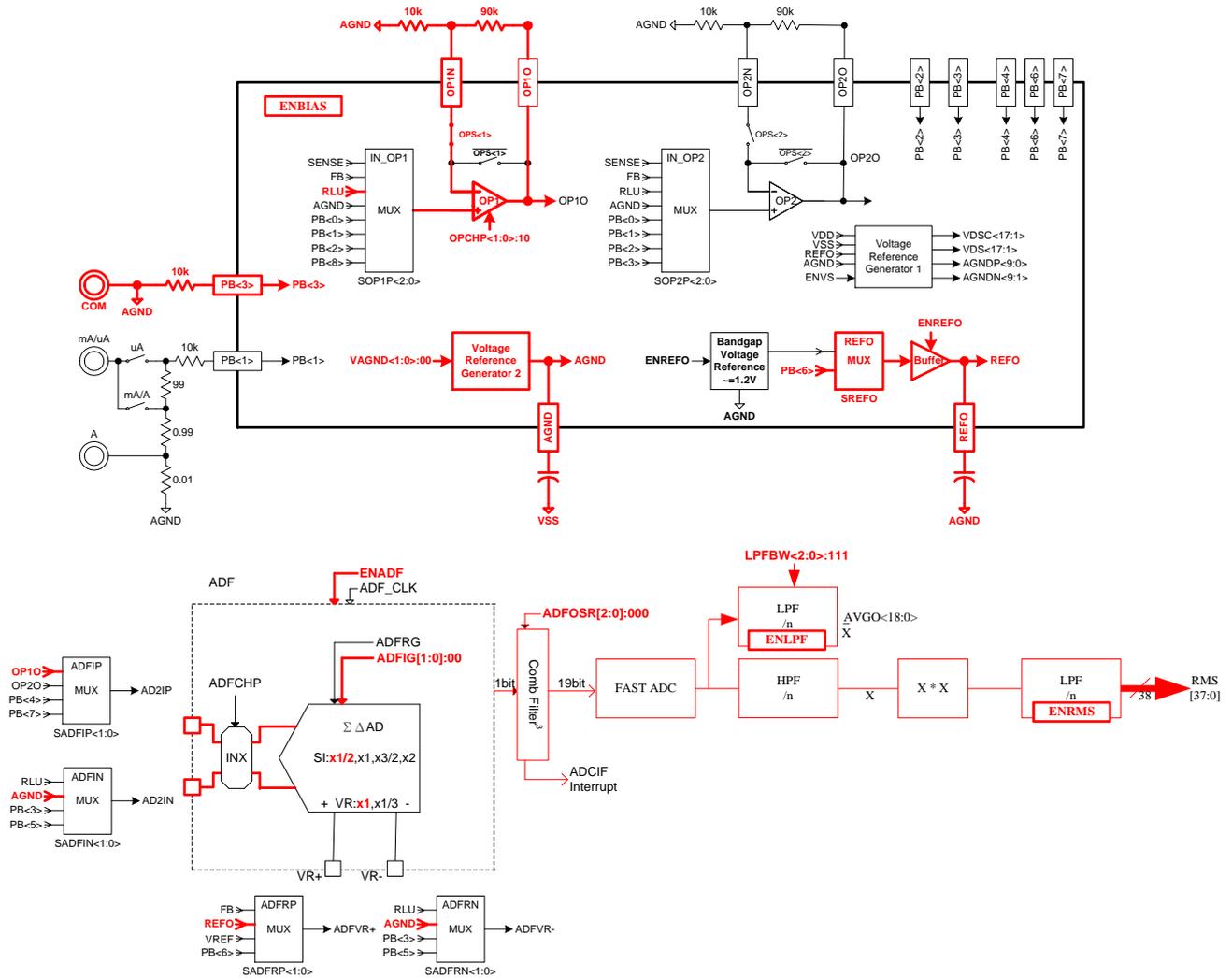
2.2. AC50mV Measurement Network Configuration



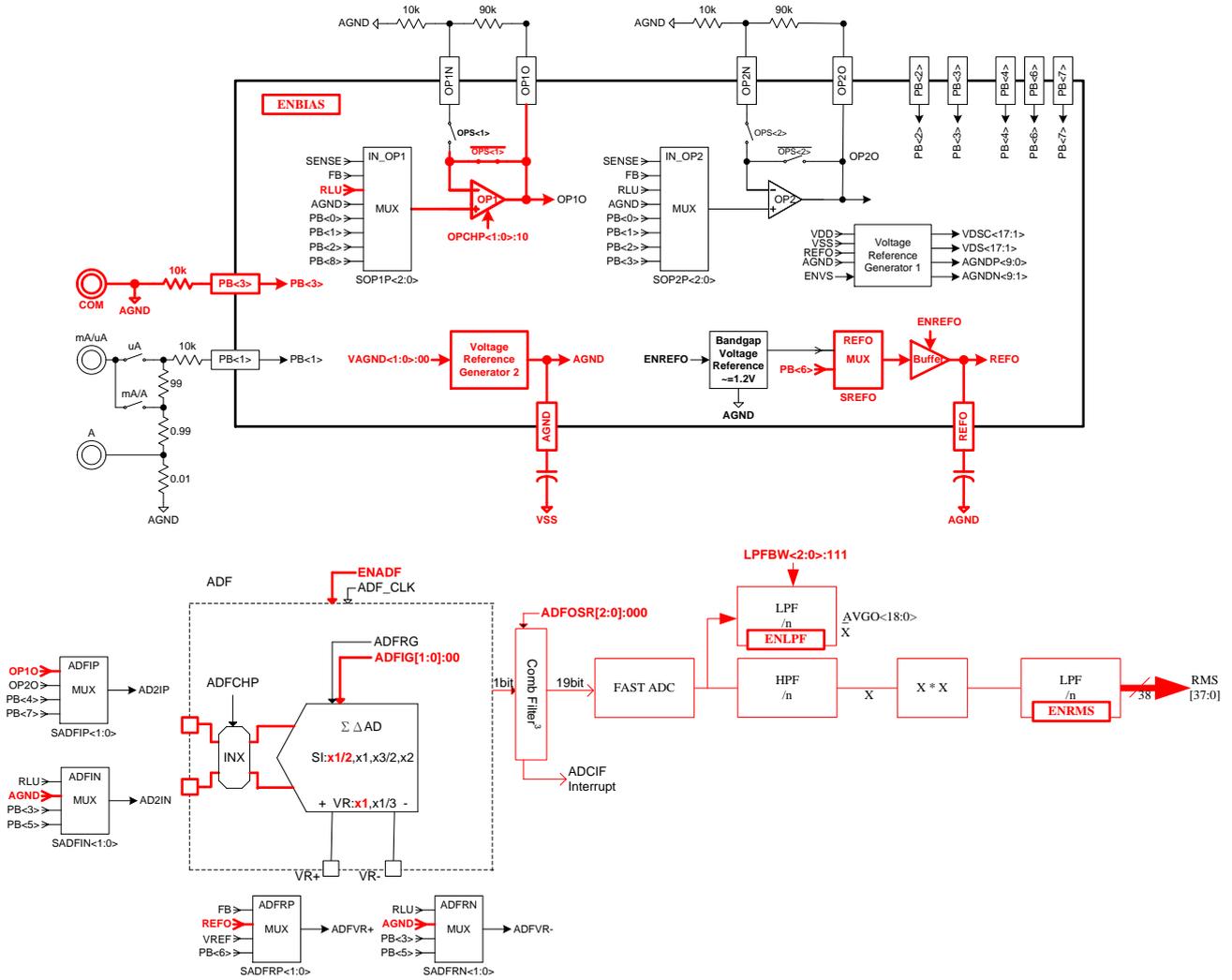
2.3. AC500mV Measurement Network Configuration



3.2. 50V Input Network Configuration


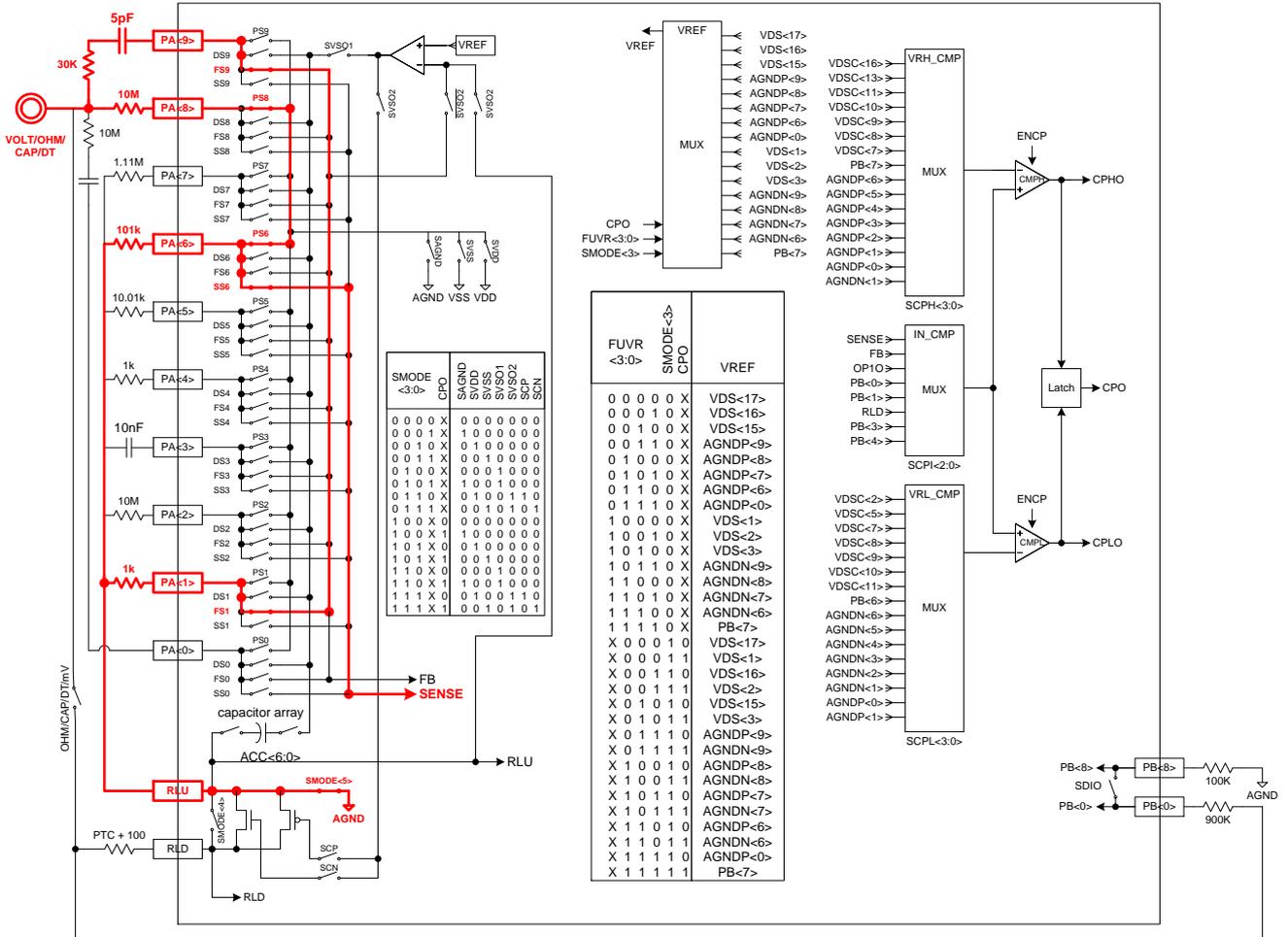


3.3. 500V Input Network Configuration

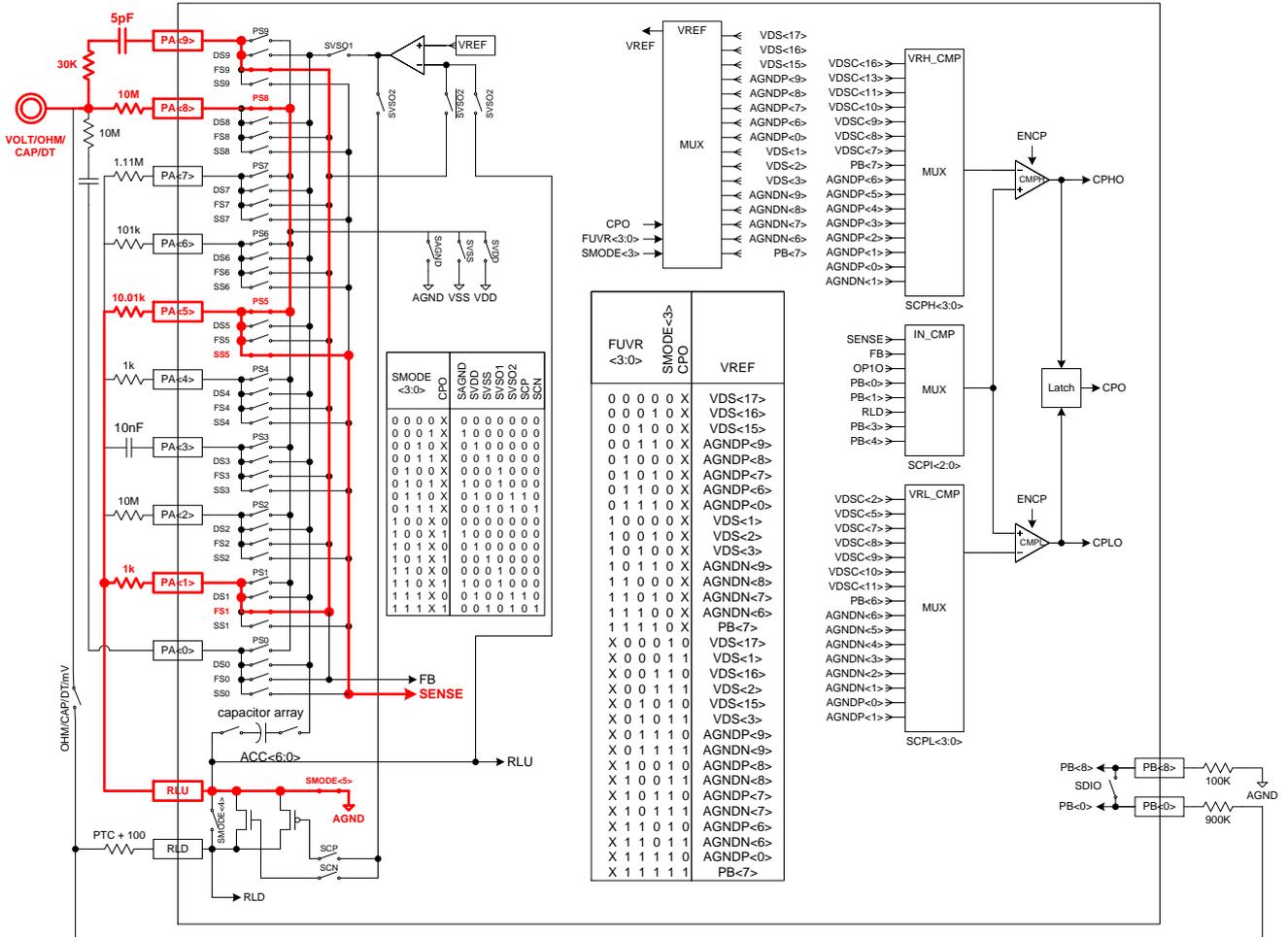

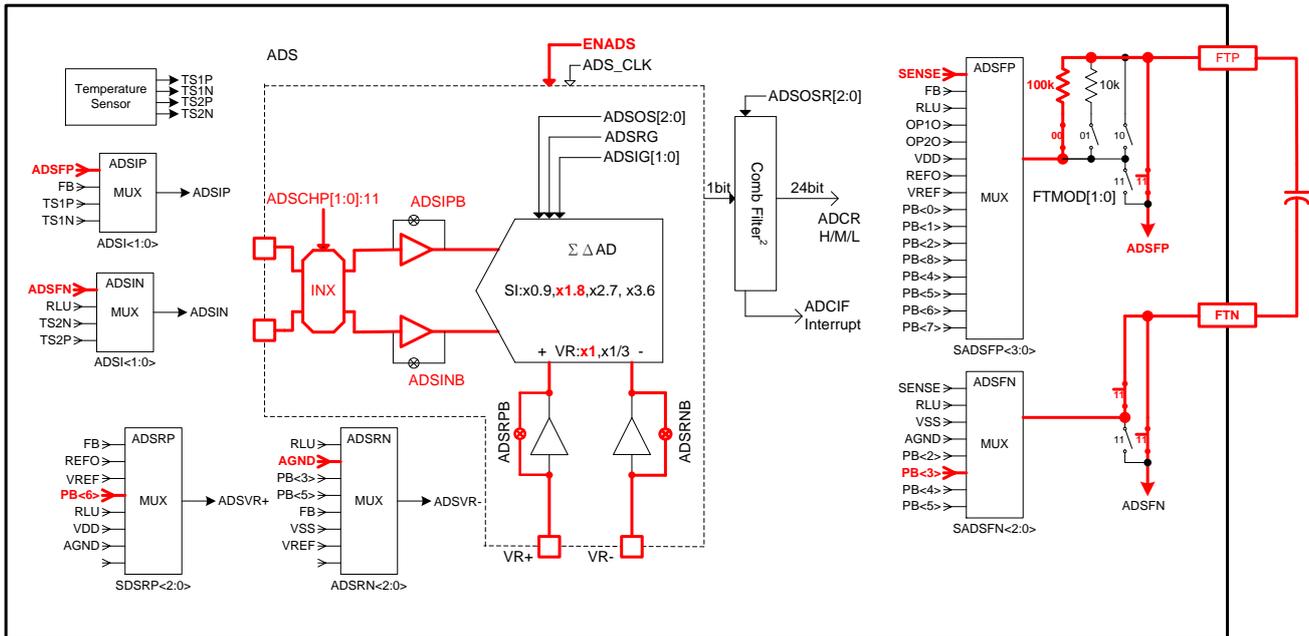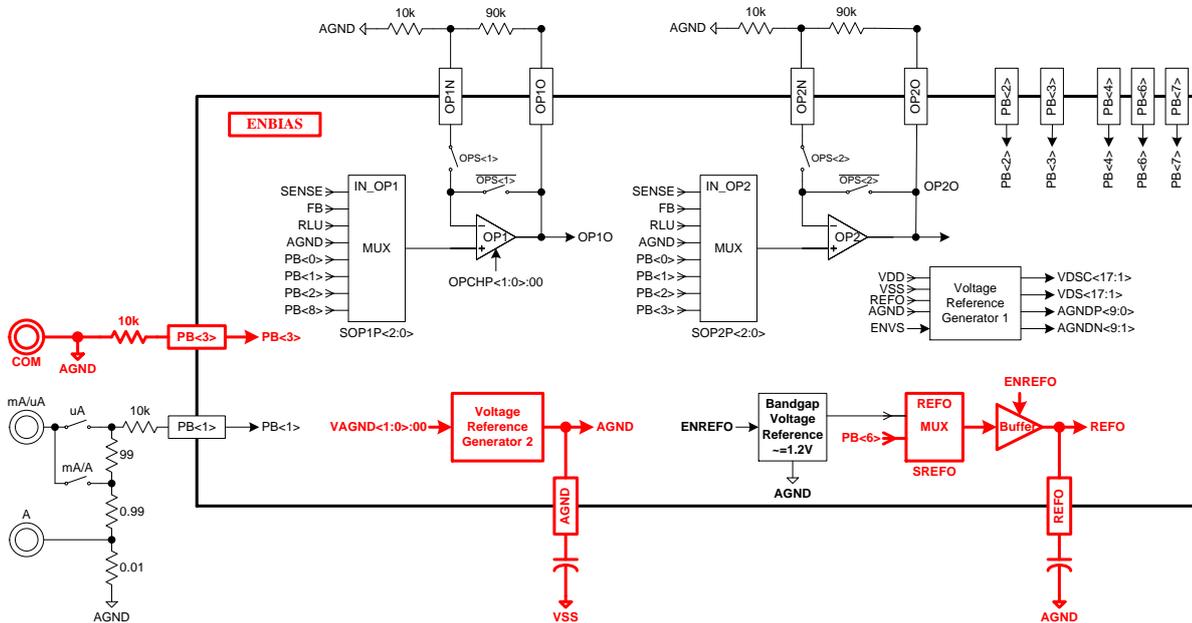3.5. DC5V~1000V Measurement Network Configuration

Main function of Chopper is to reduce DC Offset.



4. ACV

30KΩ resistor and 5pF capacitor of the input end is to compensate ACV frequency. When a part of ranges are not in use, it is recommended to connect to ground and its input divider of voltage range is shown in below equation :

$$5V_Range \Rightarrow V_{IN} \times \frac{1.111M\Omega}{10M\Omega + 1.111M\Omega} = \frac{V_{IN}}{10}$$

$$50V_Range \Rightarrow V_{IN} \times \frac{101.01K\Omega}{10M\Omega + 101.01K\Omega} = \frac{V_{IN}}{100}$$

$$500V_Range \Rightarrow V_{IN} \times \frac{10.01K\Omega}{10M\Omega + 10.01K\Omega} = \frac{V_{IN}}{1000}$$

$$1000V_Range \Rightarrow V_{IN} \times \frac{1K\Omega}{10M\Omega + 1K\Omega} = \frac{V_{IN}}{10000}$$

HY313x has two sets OPA that can be used to amplify 10 times of signal, realizing 500mV measurement by collocating with 5V network configurations.

Digital ACV bandwidth compensation capacitor equation is as follows :

$$Capacitor\ array = \sum_{n=0}^6 ACC < n > \times 2^n \times 0.2\ pF$$

Capacitance value of every Bit: (Bit = 0 or 1) x 2ⁿ x 0.2pF. Calculated capacitance value result of every Bit is shown in below table.

(unit : pF)

ACC<6:0> = n	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
ACC<n>	0/1	0/1	0/1	0/1	0/1	0/1	0/1
Capacitance Value	12.8	6.4	3.2	1.6	0.8	0.4	0.2

Example 1:

Supposed ACC<6:0>=1010101,

Then total compensation capacitance value:

$$= (1 \times 2^6 \times 0.2) + (0 \times 2^5 \times 0.2) + (1 \times 2^4 \times 0.2) + (0 \times 2^3 \times 0.2) + (1 \times 2^2 \times 0.2) + (0 \times 2^1 \times 0.2) + (1 \times 2^0 \times 0.2)$$

$$= 12.8 + 0 + 3.2 + 0 + 0.8 + 0 + 0.2$$

$$= 17\ pF$$

Example 2:

Supposed ACC<6:0>=1100011 ,


Then total compensation capacitance value:

$$= (1 \times 2^6 \times 0.2) + (1 \times 2^5 \times 0.2) + (0 \times 2^4 \times 0.2) + (0 \times 2^3 \times 0.2) + (0 \times 2^2 \times 0.2) + (1 \times 2^1 \times 0.2) + (1 \times 2^0 \times 0.2)$$


$$= 12.8 + 6.4 + 0 + 0 + 0 + 0.4 + 0.2$$

$$= 19.8\ pF$$


4.1. 5V Input Network Configuration

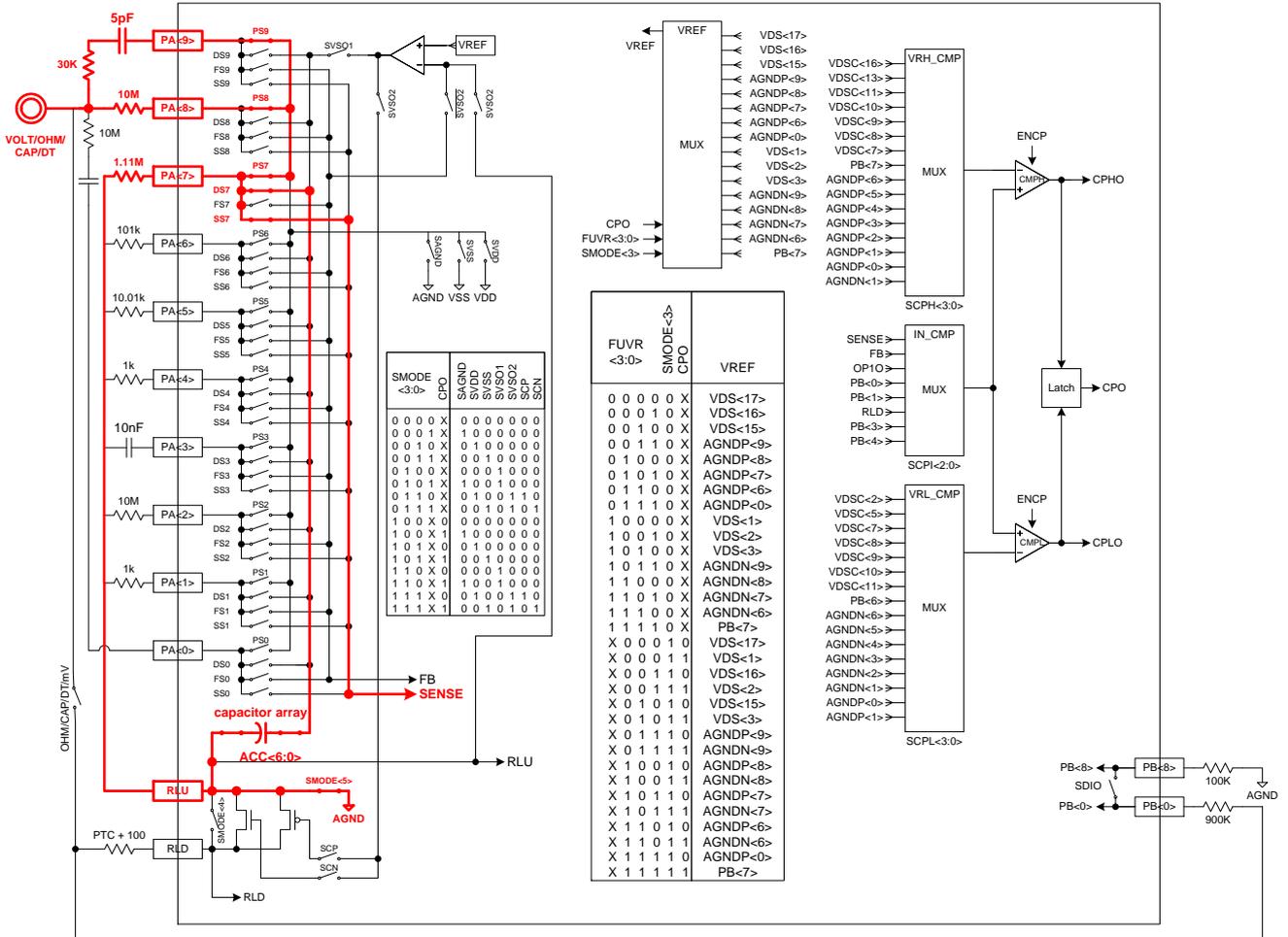

4.2. 50V Input Network Configuration

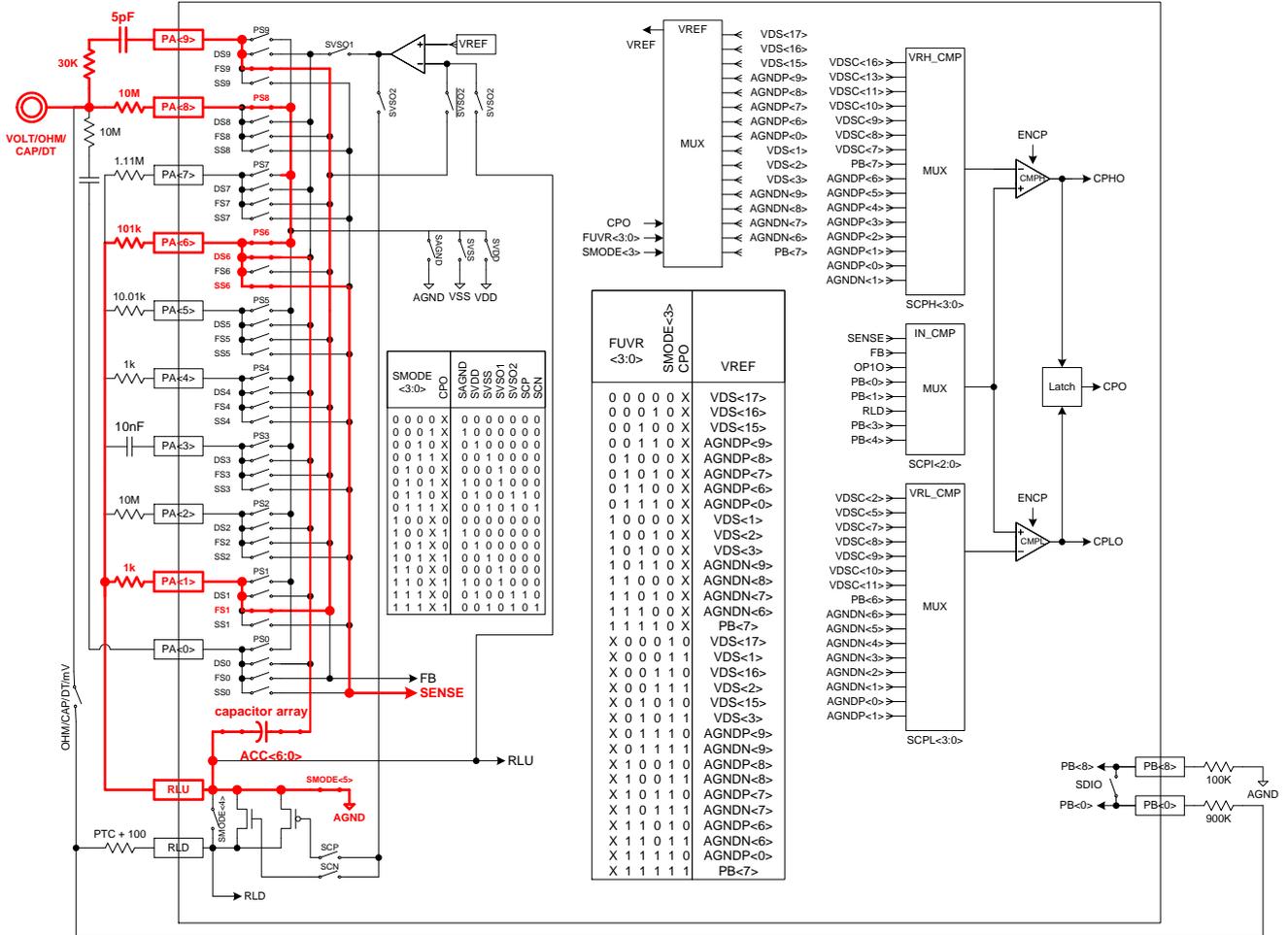


4.3. 500V Input Network Configuration

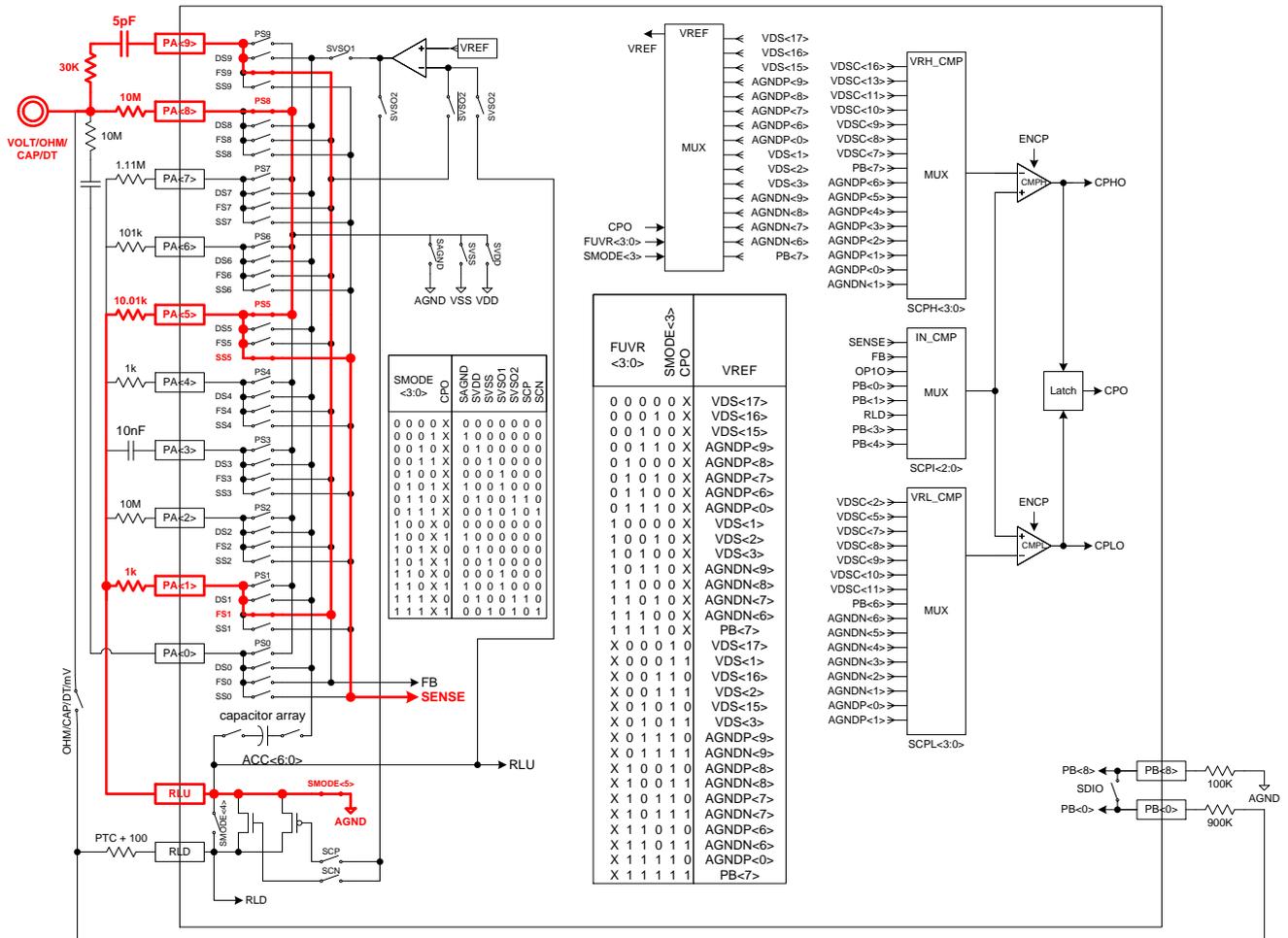

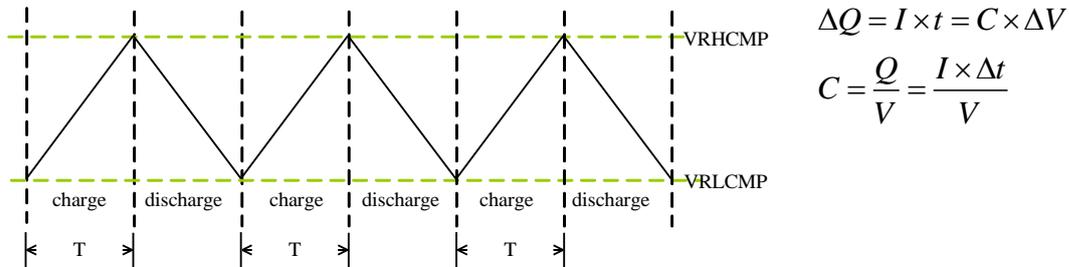5. Capacitance


There are two ways to measure capacitance, constant voltage and constant current output mode. Under low capacitance ($<1 \mu\text{F}$), users need to use constant voltage output mode for testing whereas using constant current output mode to test high capacitance ($>1 \mu\text{F}$). Capacitance measurement uses charge/discharge test cycle to gain the value.




Capacitance measurement test procedure :

1. Select constant voltage (SMODE<5:0>=011010b) and constant current (SMODE<5:0>=001110b) test mode output.
2. Configure capacitor charge/discharge comparison voltage (VRHCMP、VRLCMP) and the actual charge/discharge of capacitor is decided by comparator, ACPO.
3. Configure CTA<23:8> initial value of Frequency Counter. When INTF2 register, CTF bit is 1, CTC<23:0> divided by CTB<23:0> to gain the cycle length.

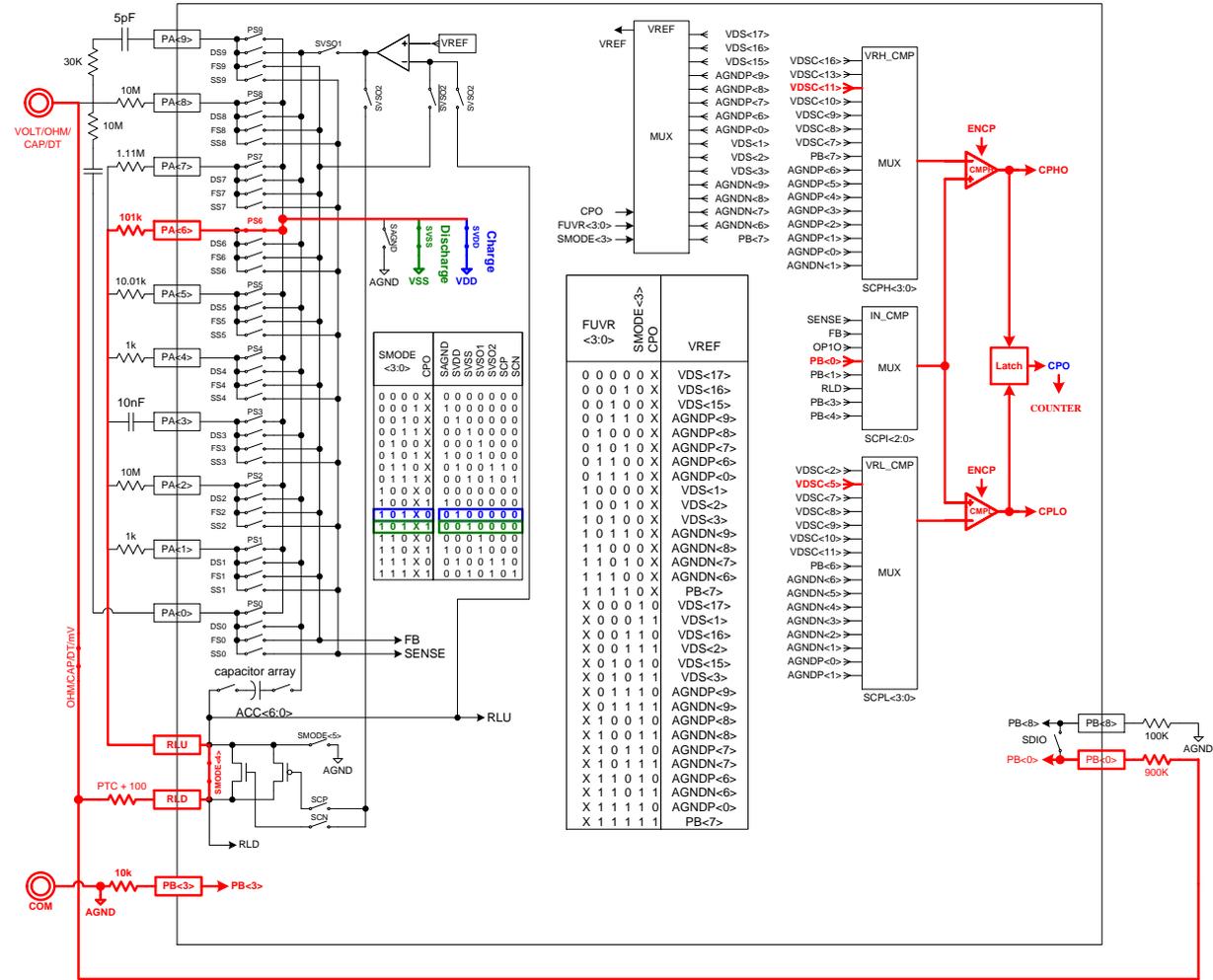
5.1. 50-500nF (Constant Voltage Charge/Discharge Measurement)



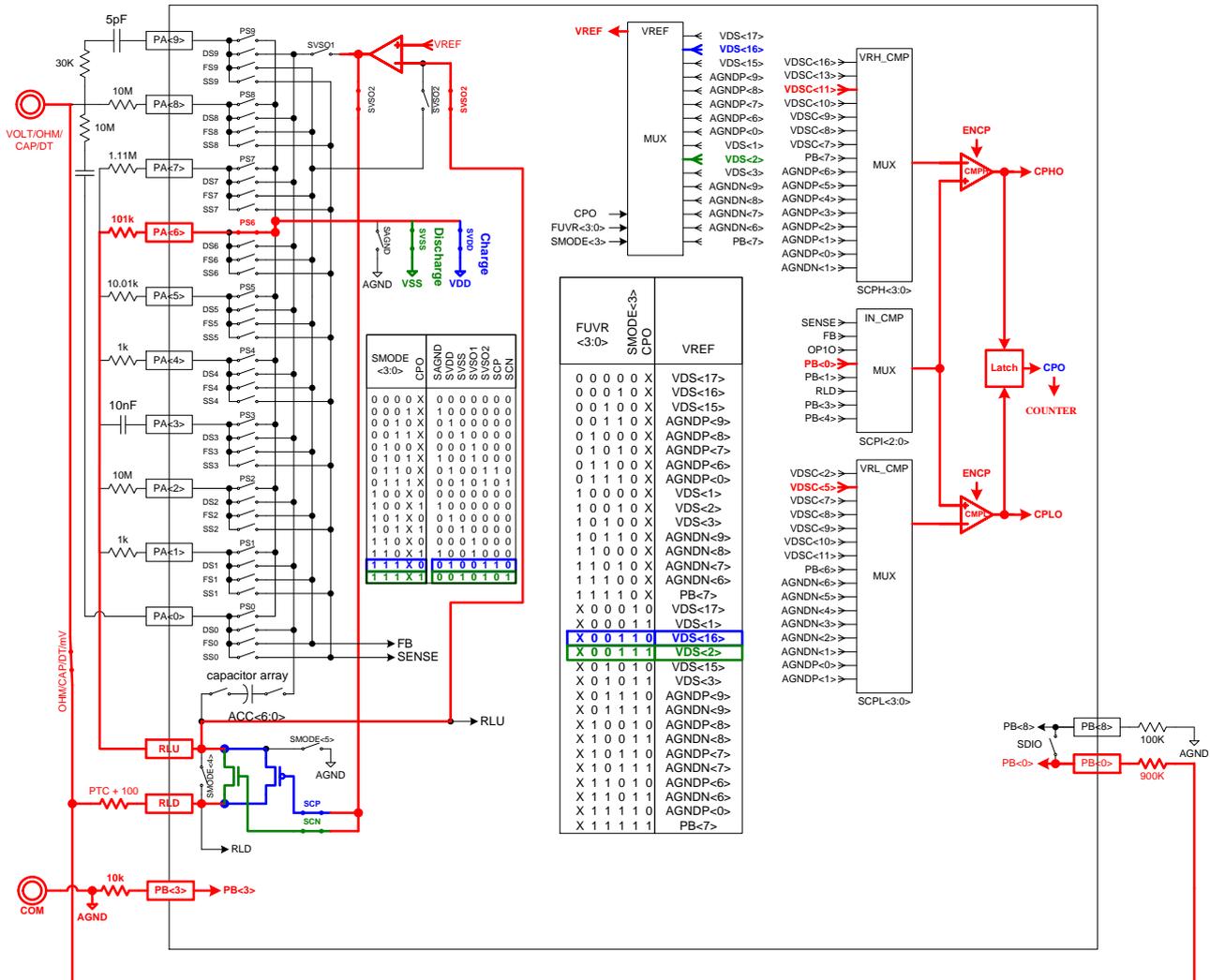5.2. 5uF-50uF (Constant Current Charge/Discharge Measurement)




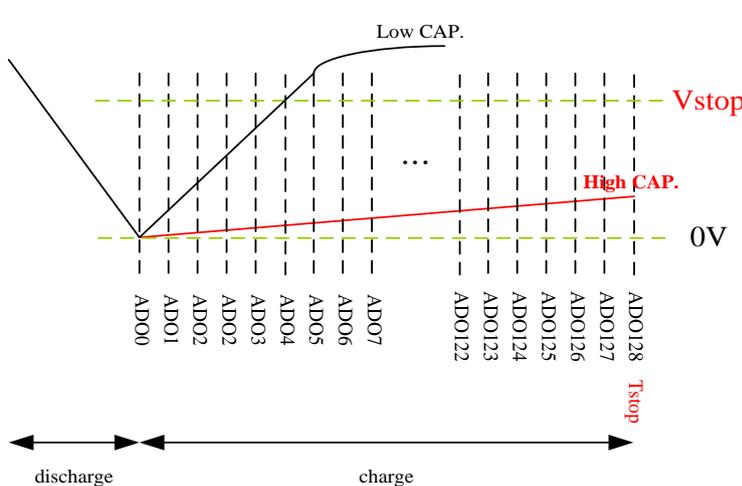500uF~50mF capacitors require longer charge/discharge time, the only change of different ranges is the output current. Users can take the voltage difference under a fixed time (t) to gain capacitor value. The change of capacitor value and voltage value is an inverse ratio.




$$C = \frac{Q}{V} = I \times \frac{\Delta t}{\Delta V}$$


5.3. 500uF(Charge)

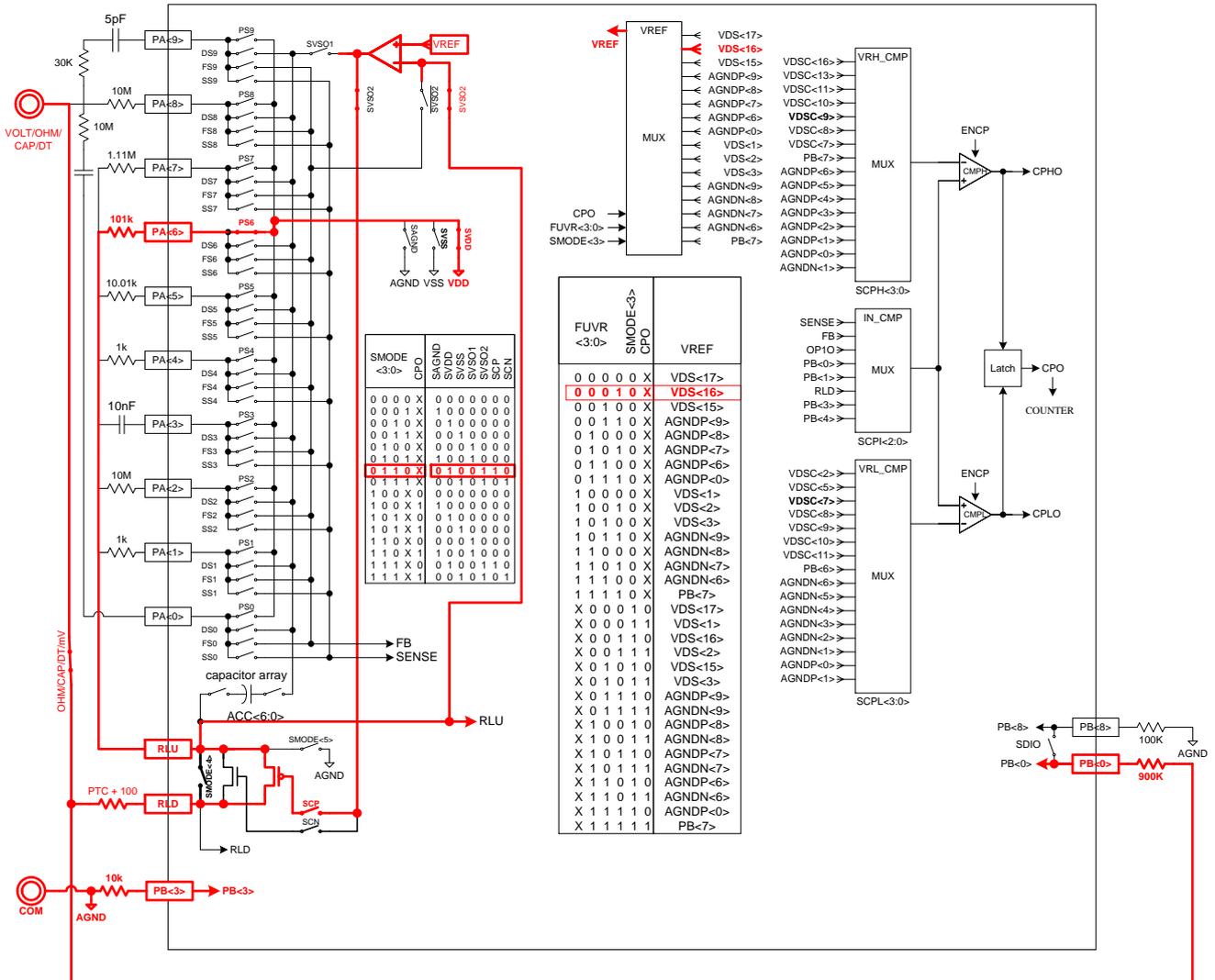

5.4. 5mF-50mF(Charge)

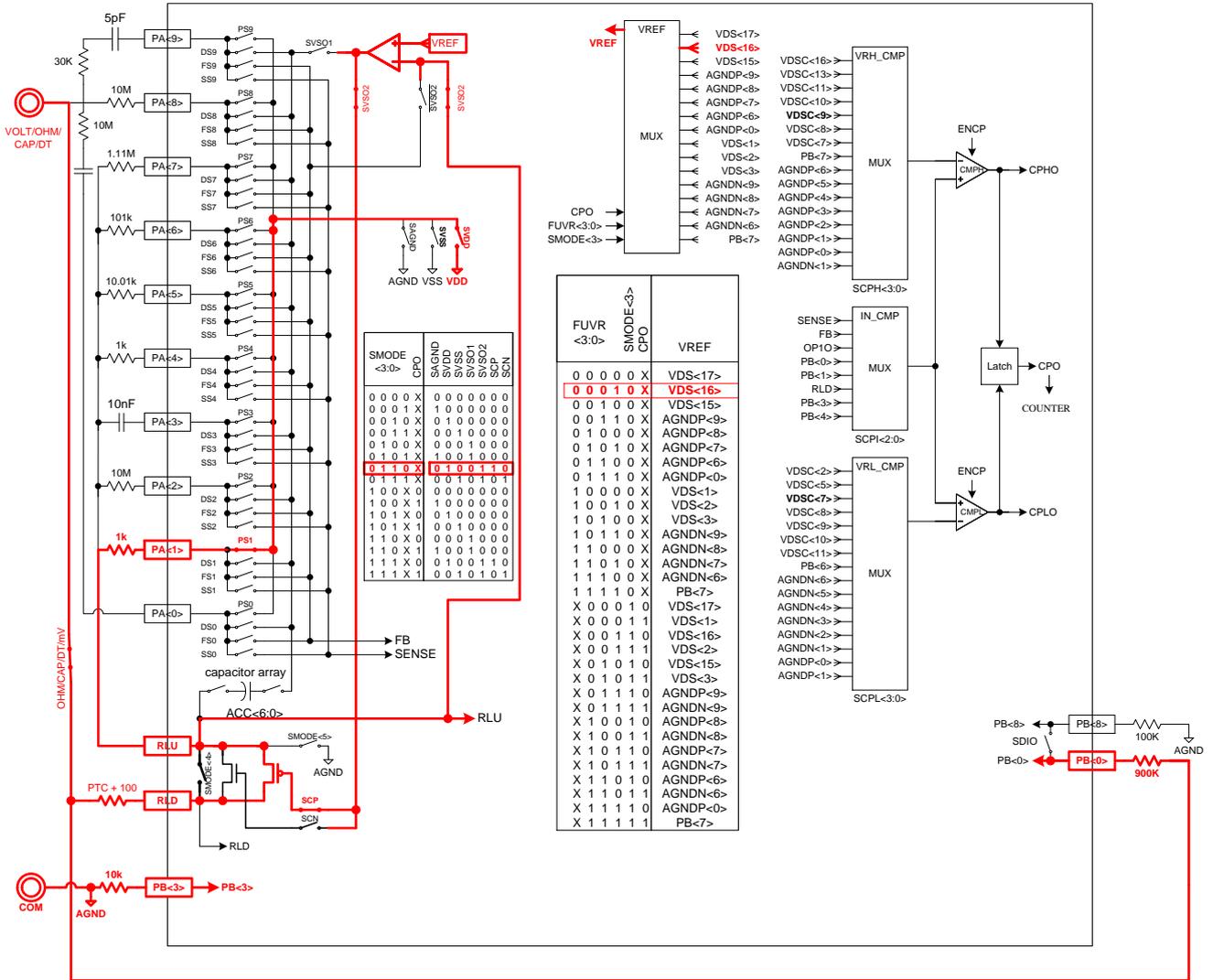


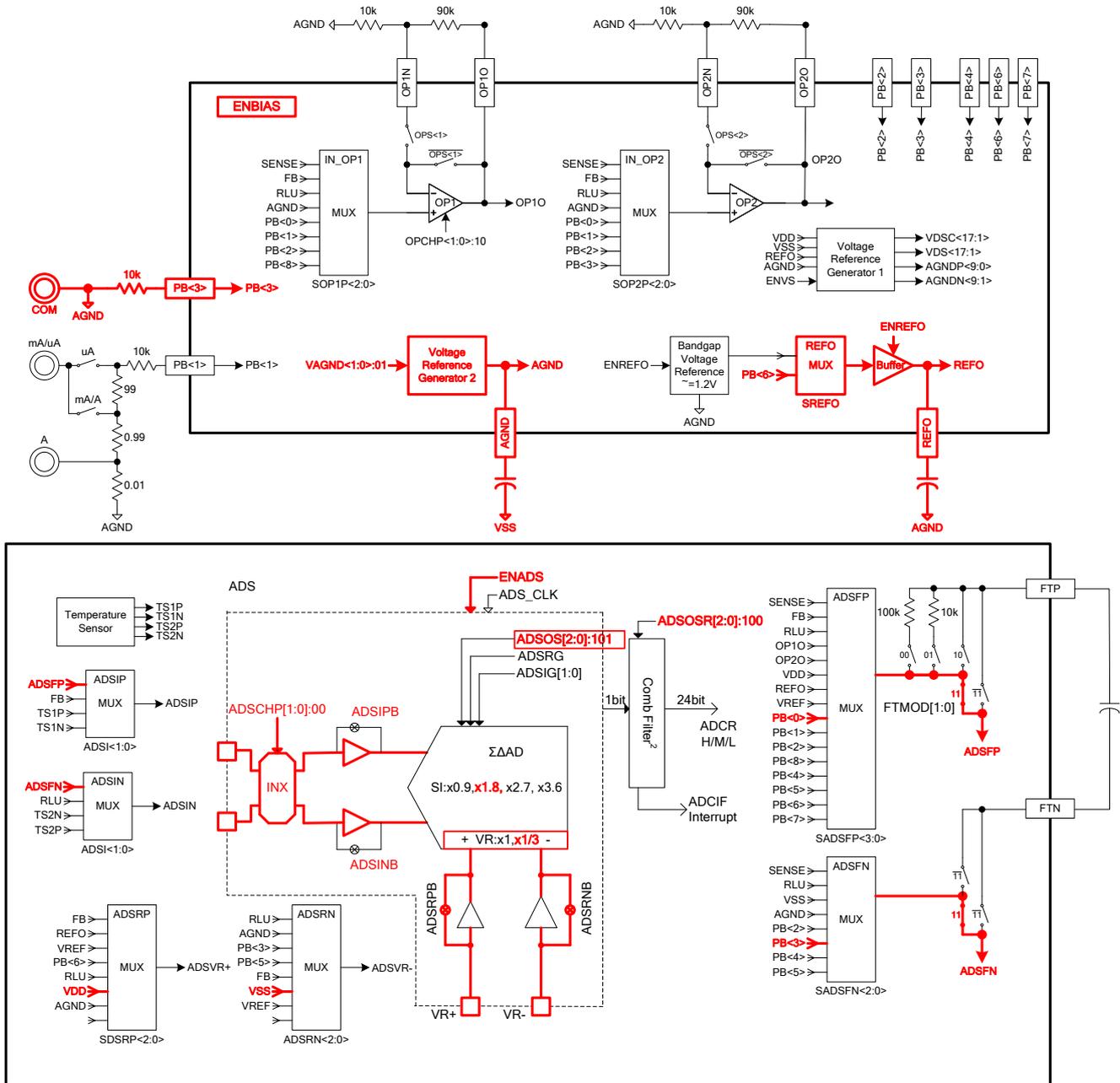5.5. 500uF~50mF Measurement Network Configuration




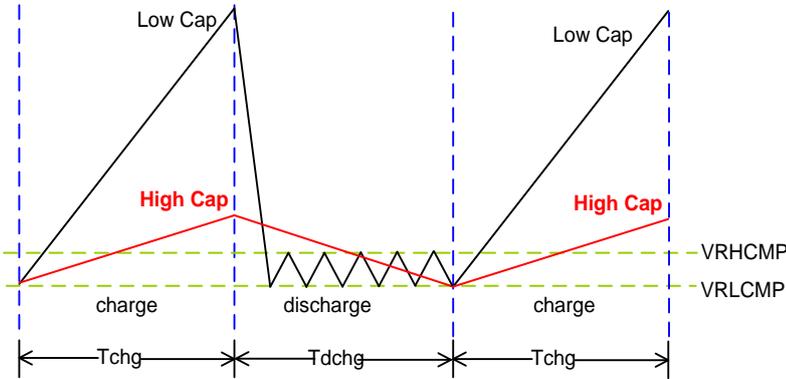5.6. Discharge (500uF~50mF)


When discharging, set SMODE<5:0> to 001110b and the comparator to be close to AGND, so that the capacitor discharges itself to 0V. Regardless of the capacitance, the charging and discharging times are fixed.



◀ Charging and discharging diagram

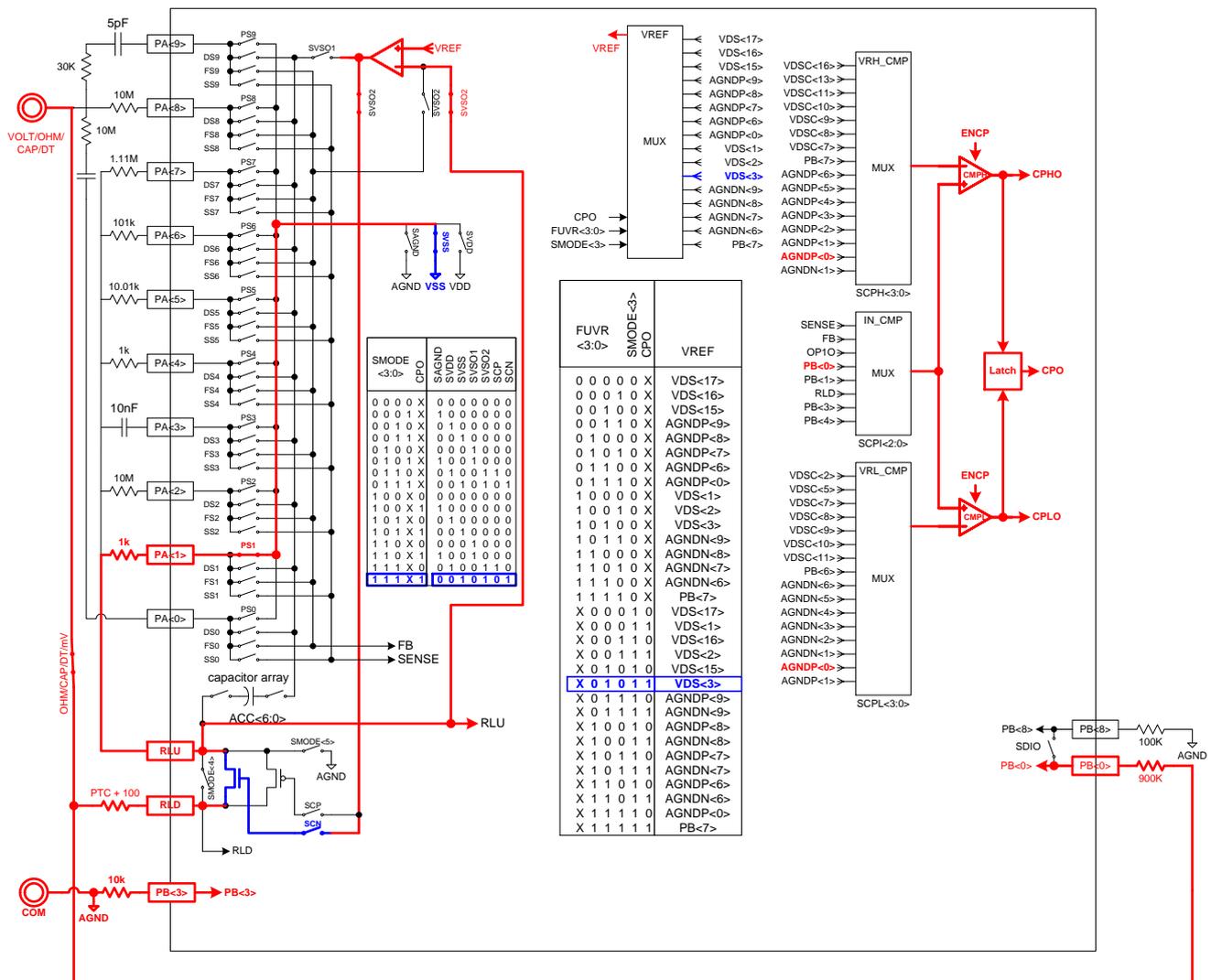


HY313X Configurations

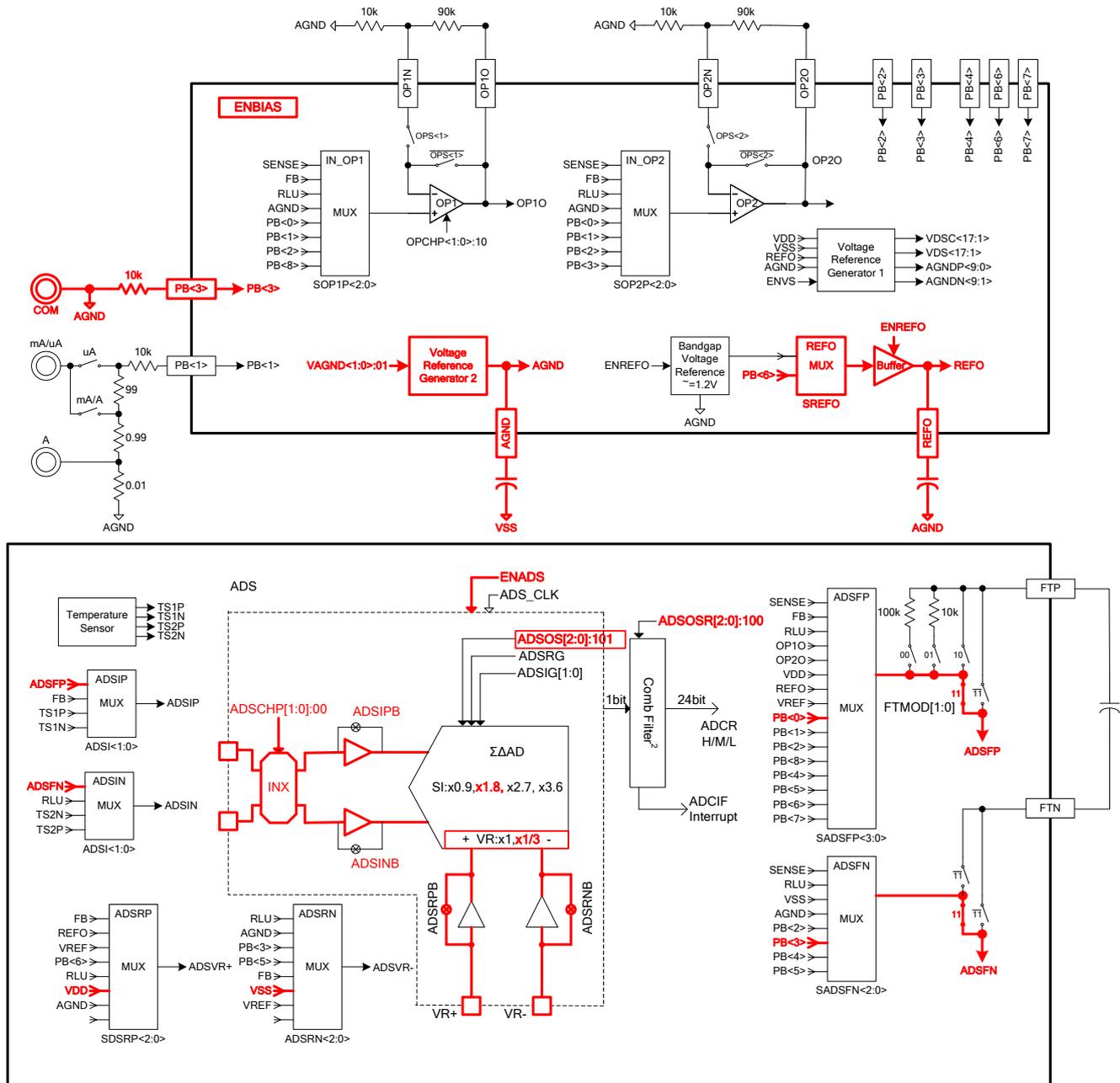

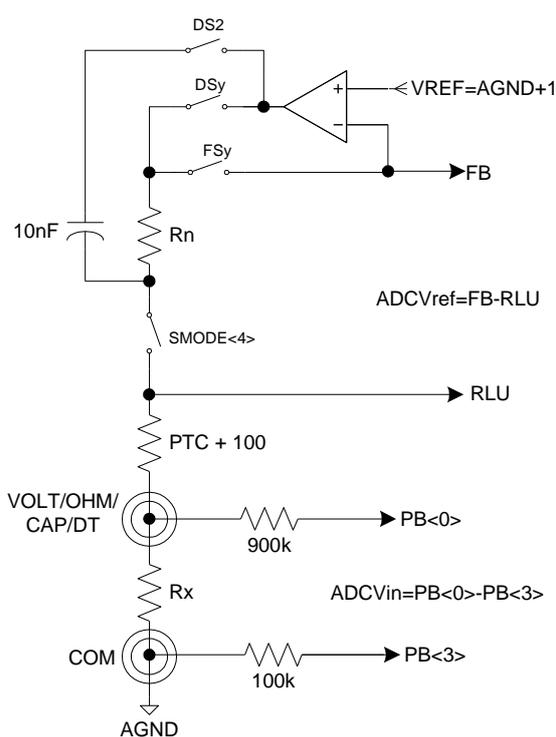6. Resistor

The chip offers two ways to measure resistor, constant voltage and constant current measurement and different methods lead to diverse results.

Constant voltage or ratio resistor measurement design must input ADC signal and open reference voltage input buffer when measuring high resistor. 3MΩ parallel connection impedance will be generated if ADC input was not opened. It is suggested to use constant current resistor measurement when design 500kΩ to 50MΩ application. The measurement equation is given below :




$$I_{Rx} = I_{Rn}$$

$$V_{Rx} = I_{Rx} \times Rx = \frac{V_{Rn}}{Rn} \times Rx$$

$$R_{READ} = \frac{V_{Rx}}{V_{Rn}} \times Full\ Scale = \frac{ADCV_{in}}{ADCV_{ref}} \times Full\ Scale$$

Constant current resistor measurement design has higher internal impedance of DS_n and SVDD electrical switches; it will have parallel connection with R_n resistor and to cause output current deviation. It is recommended to use constant voltage resistor measurement when designing 500kΩ or below applications. The measurement equation is given below :

HY313X Configurations

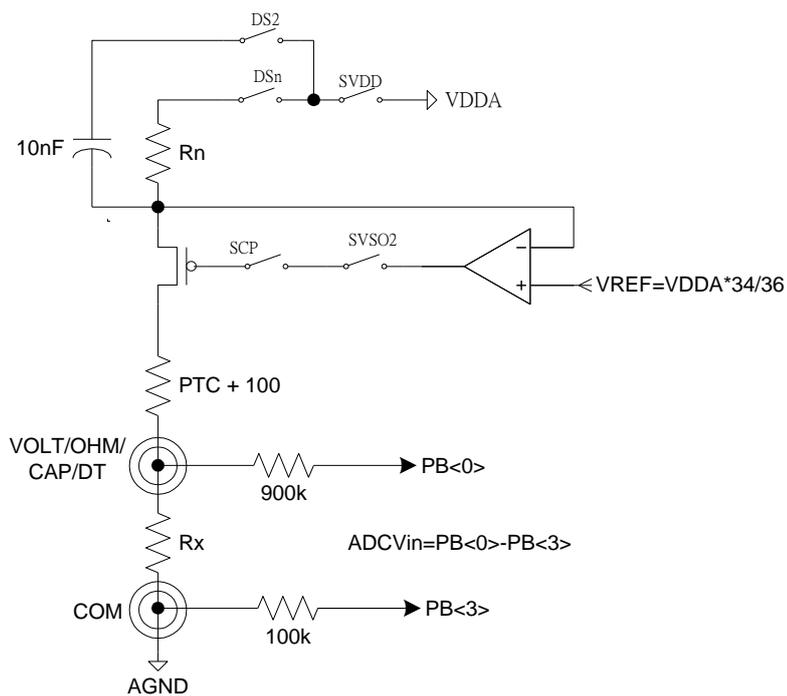


$$I_{Rx} = I_{Rn} = \frac{VDDA - VREF}{Rn}$$


$$R_{READ} = \frac{ADC_{V_{in}}}{ADC_{V_{ref}}} \times Full\ Scale$$

$$R_{READ} = \frac{Rx \times I_{Rx}}{ADC_{V_{ref}}} \times Full\ Scale$$

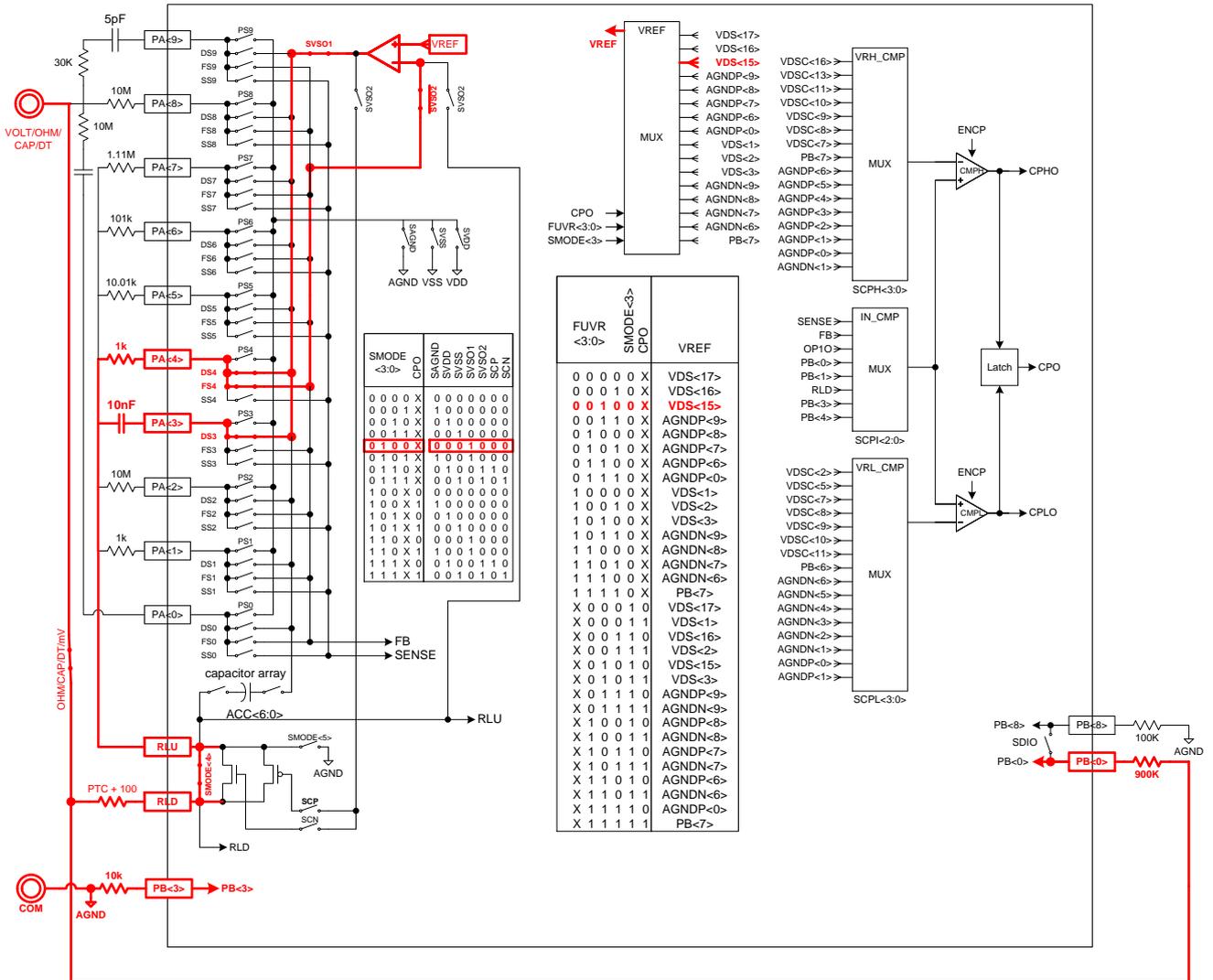
6.1. 50ohm/500ohm Input Network Configuration




6.2. 5K ohm Input Network Configuration

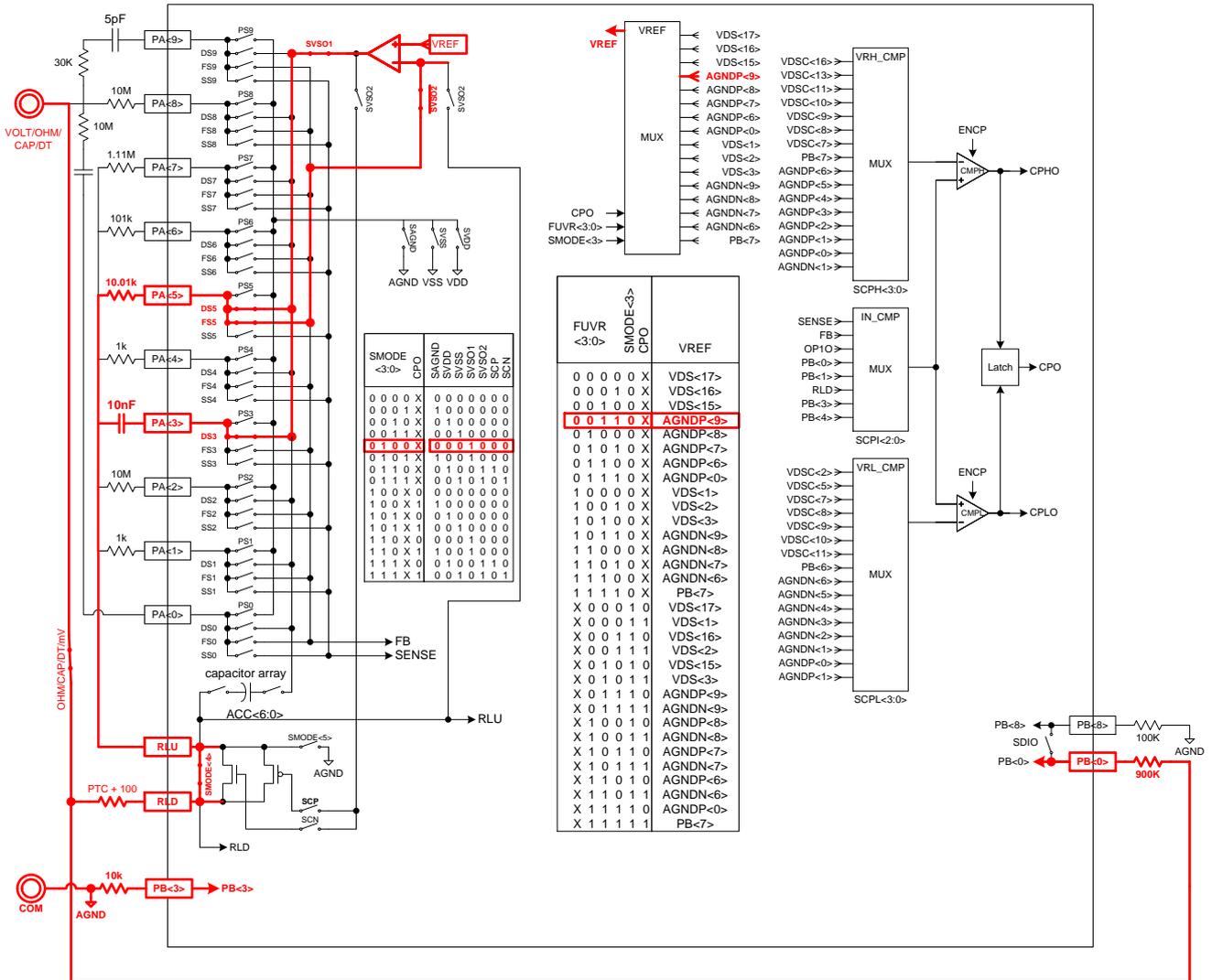

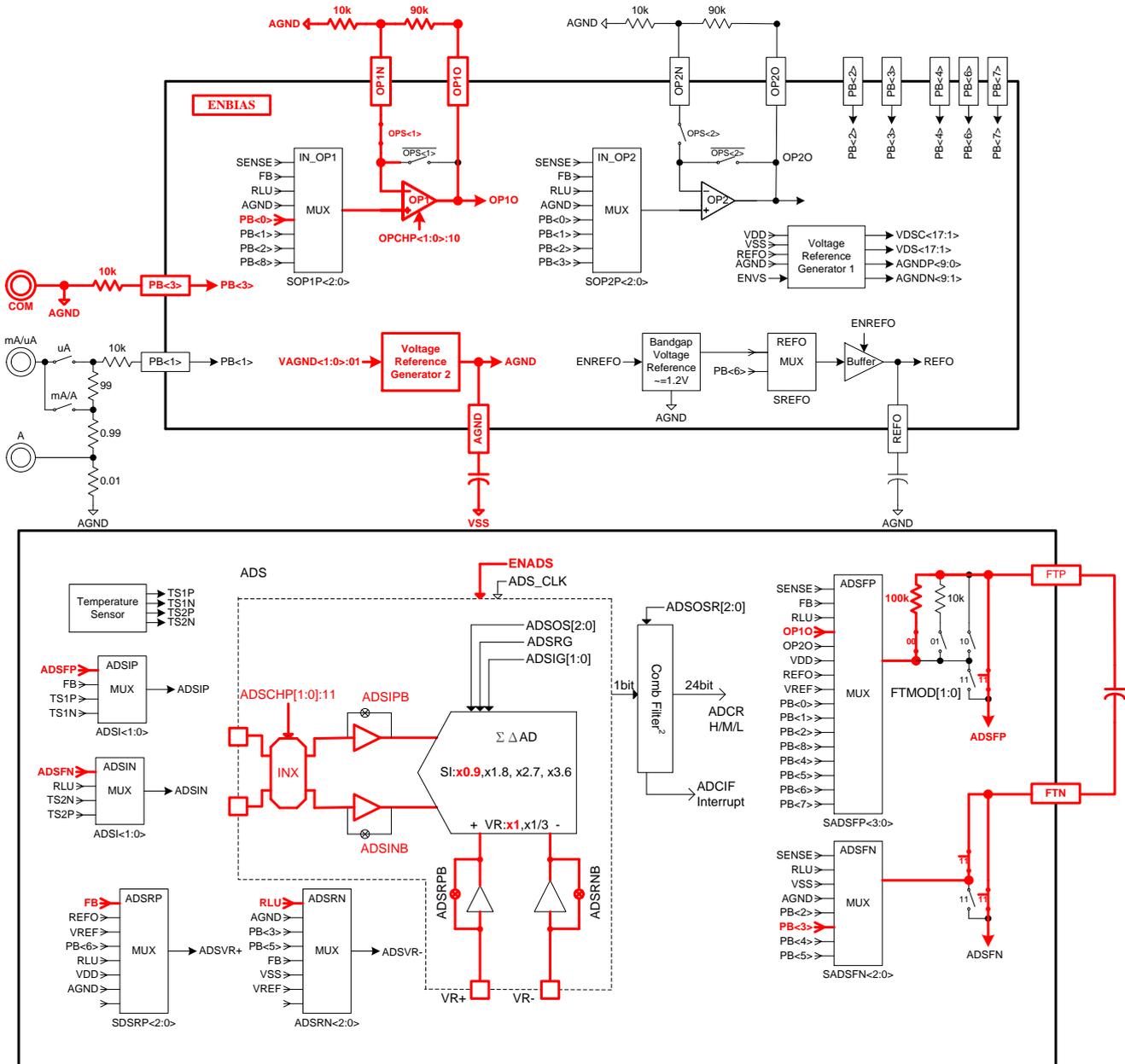
6.3. 50ohm Measurement Network Configuration



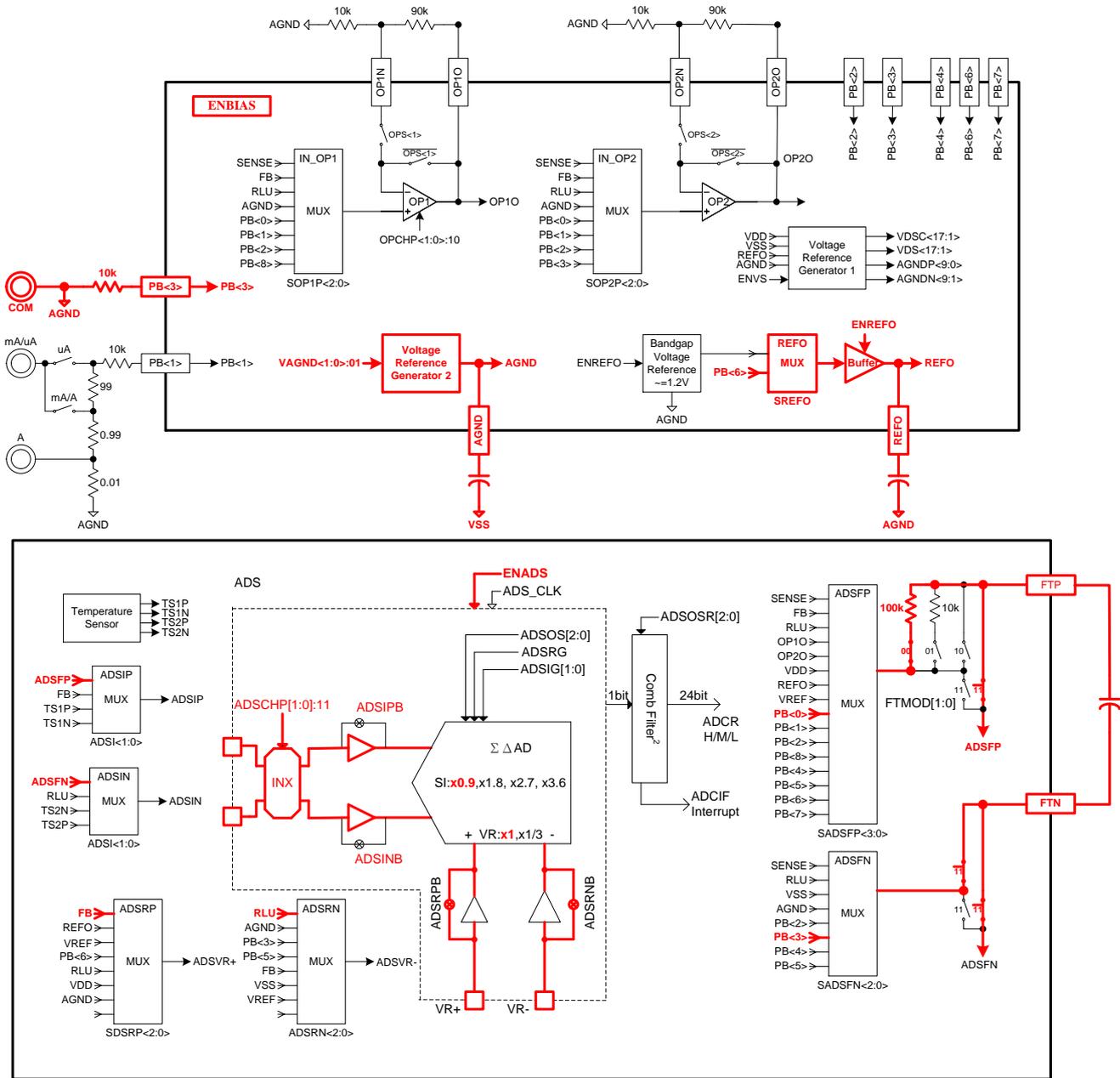
6.4. 500 ohm~50K ohm Measurement Network Configuration




6.5. 50Kohm Input Network Configuration

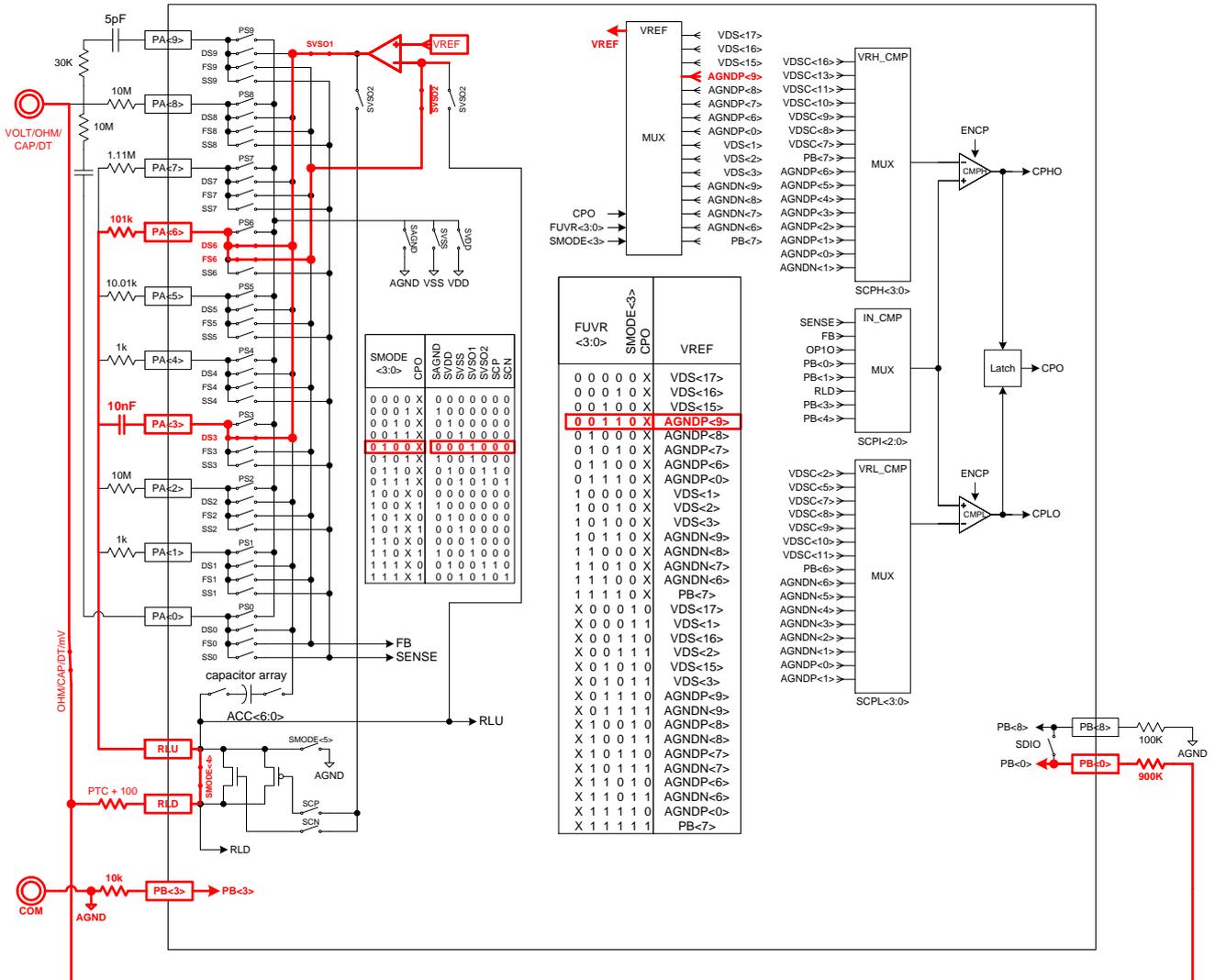


6.6. 500Kohm Input Network Configuration

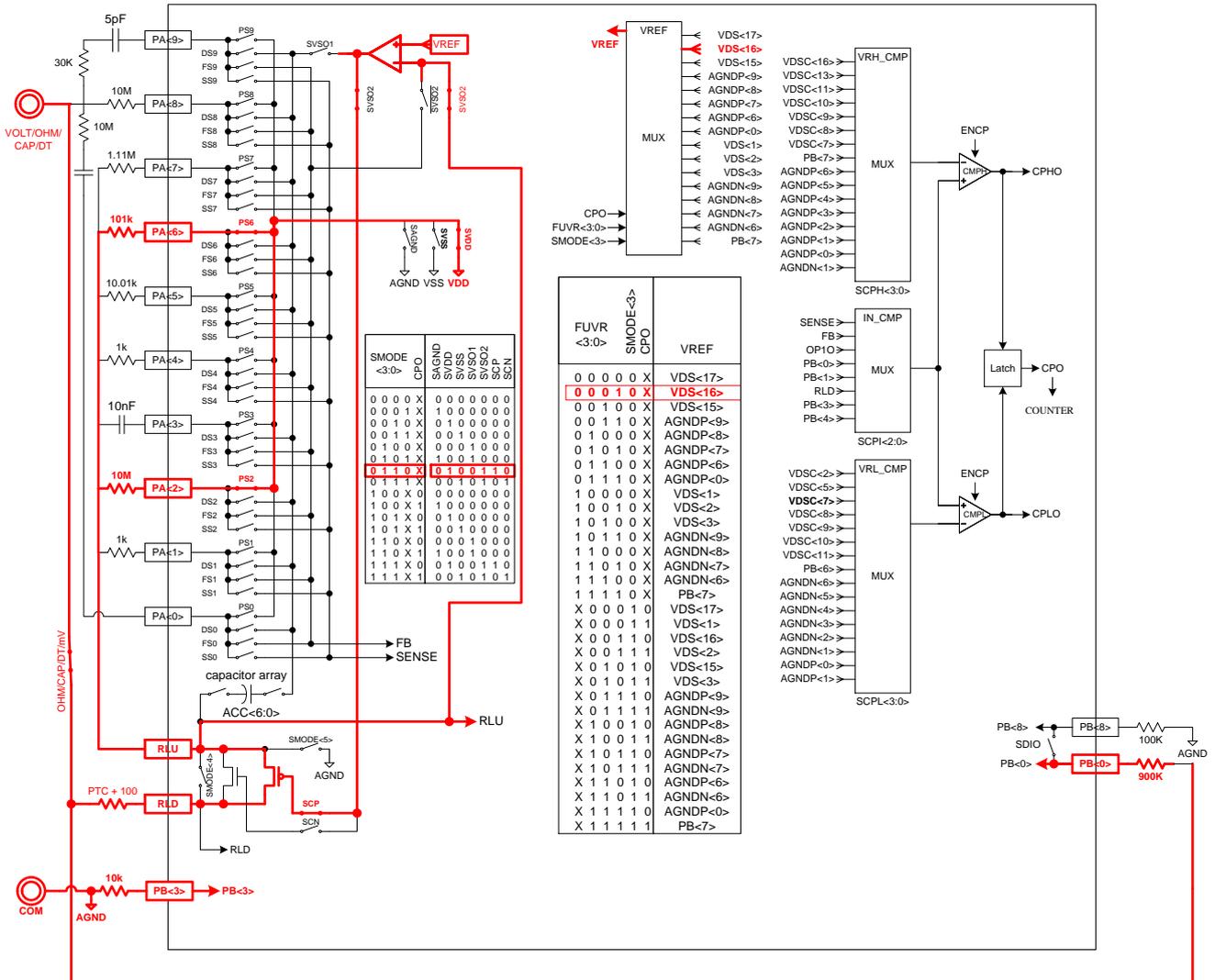



6.7. 5M ohm Input Network Configuration

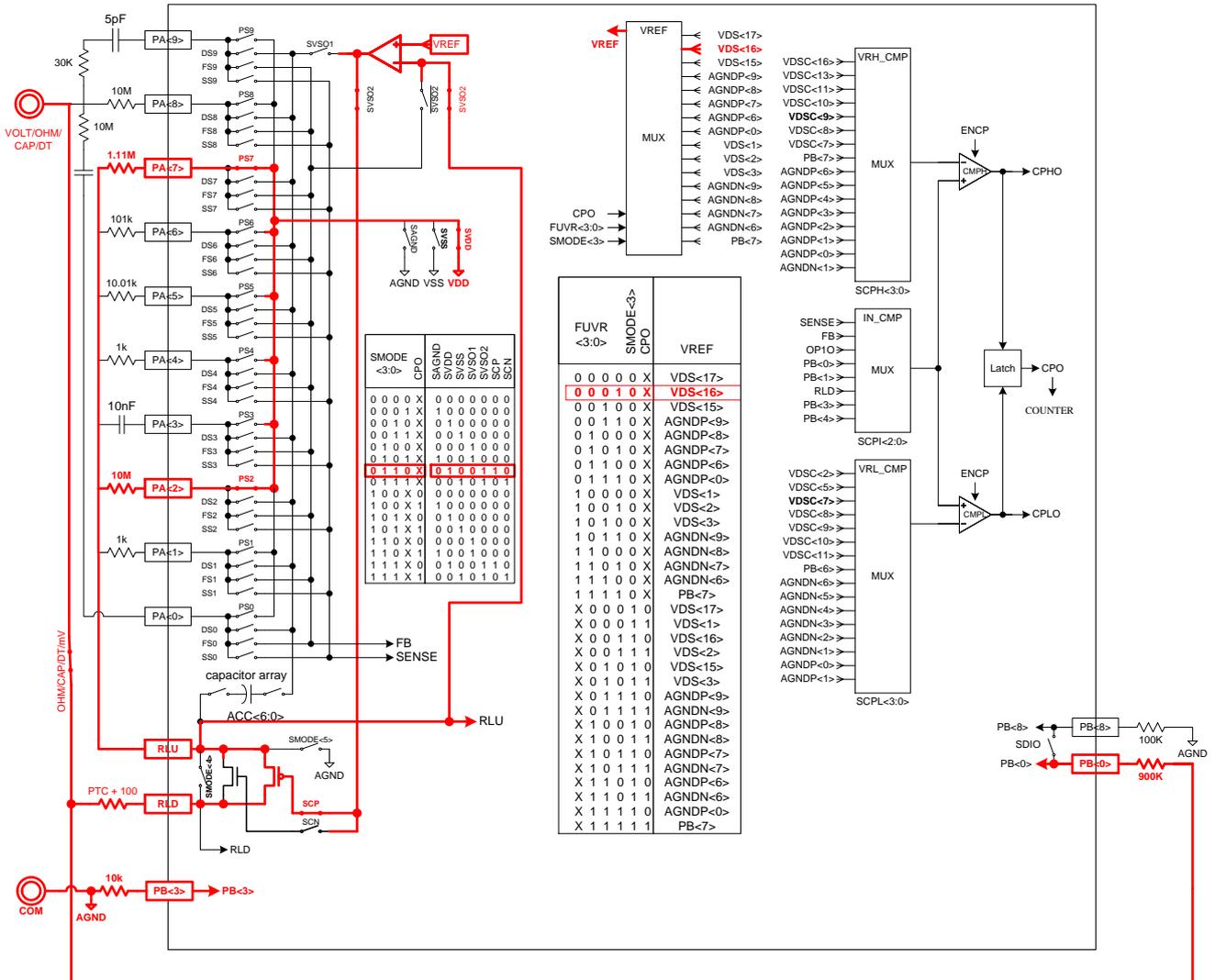

6.8. 50Mohm Input Network Configuration

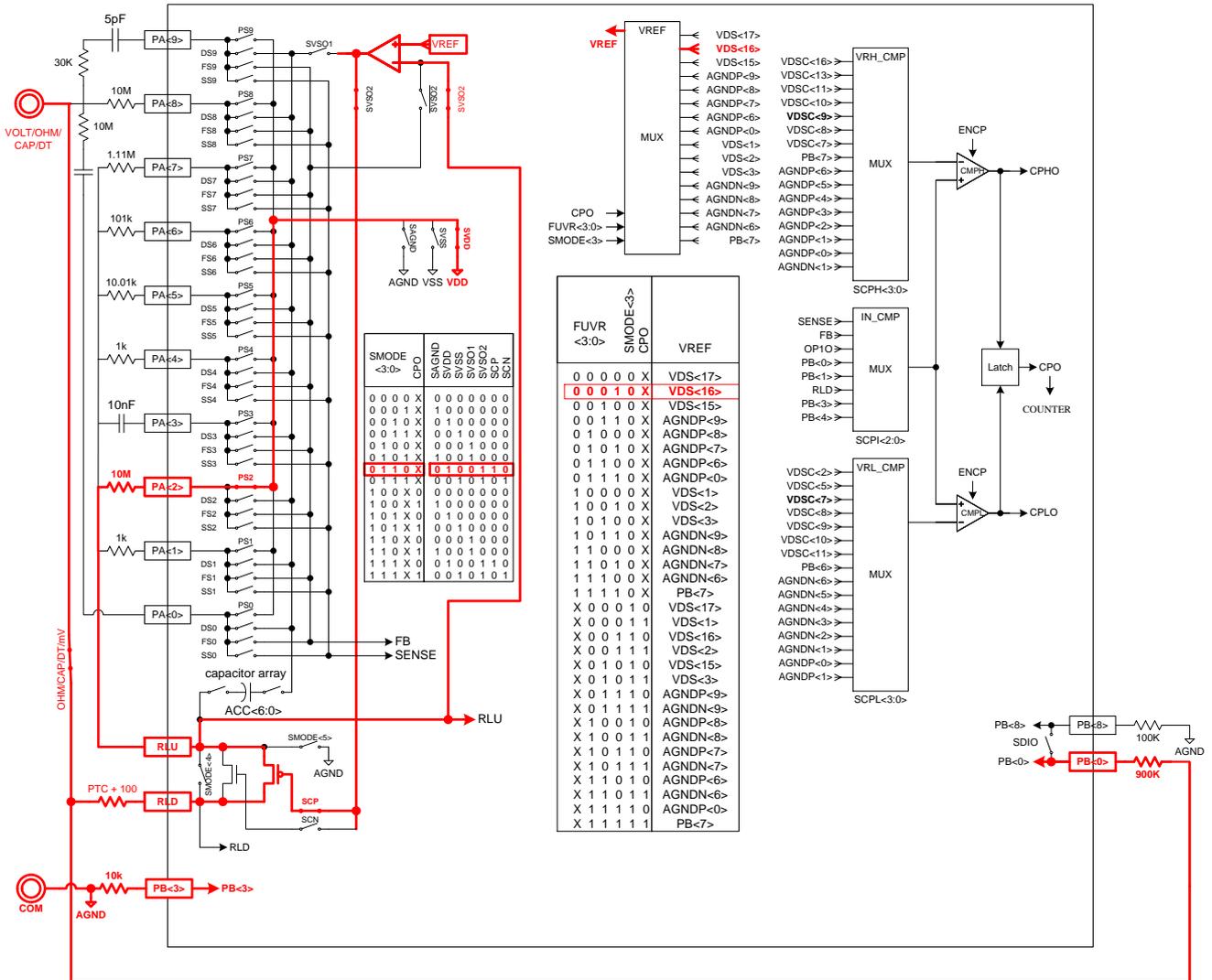

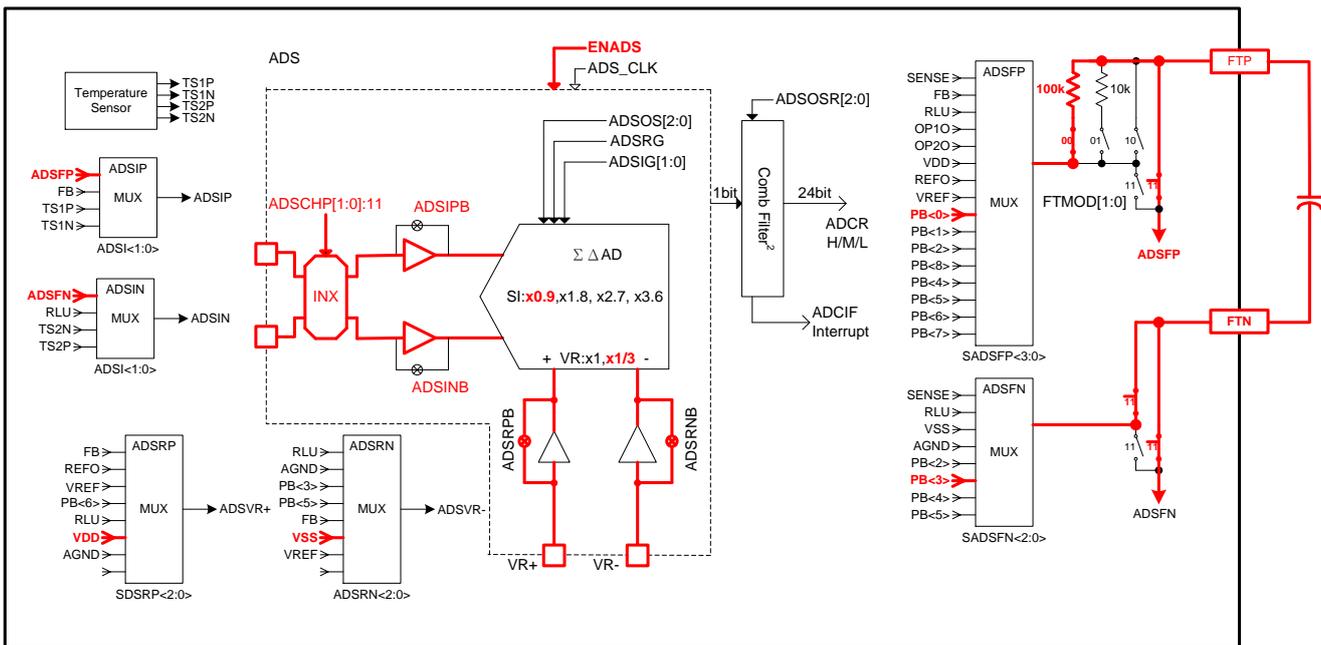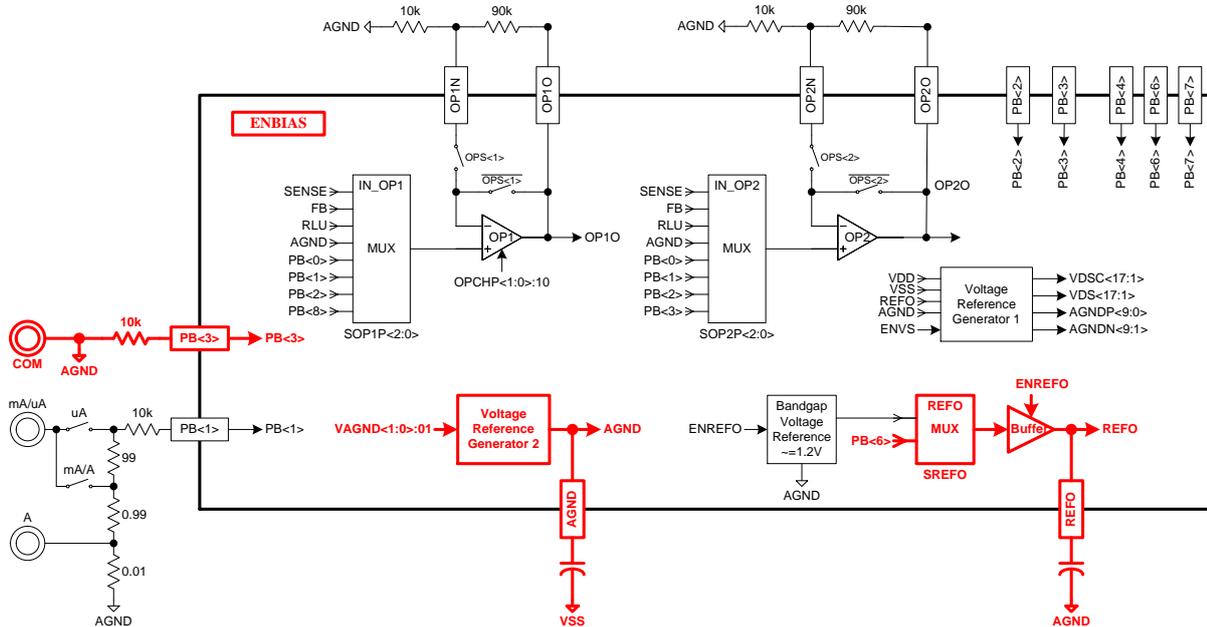6.9. 500Kohm~50Mohm Measurement Network Configuration




7. Diode


Diode function is to measure Forward Voltage or called PN Barrier Potential. This chip offers positive/negative constant current source or positive/negative constant voltage source measurement. This example illustrates positive constant current measurement.

When constant current passed through diode, both edges of component will have voltage difference. The voltage is around 0.2V~1.5V, to prevent exceeding full scale. Thus, taking 900k Ω and 100k Ω to form 10 times attenuation.

7.1. Diode Input Network Configuration

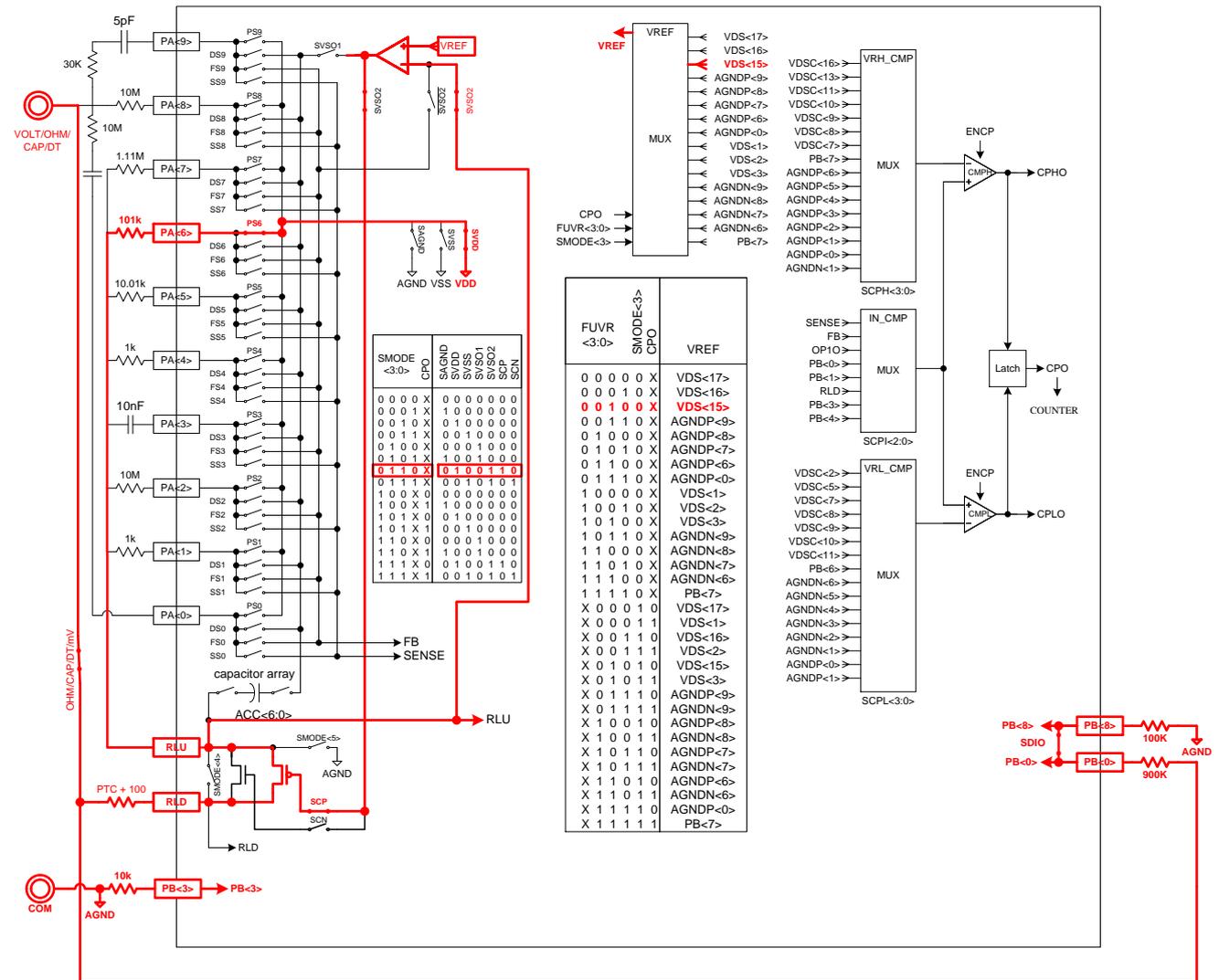


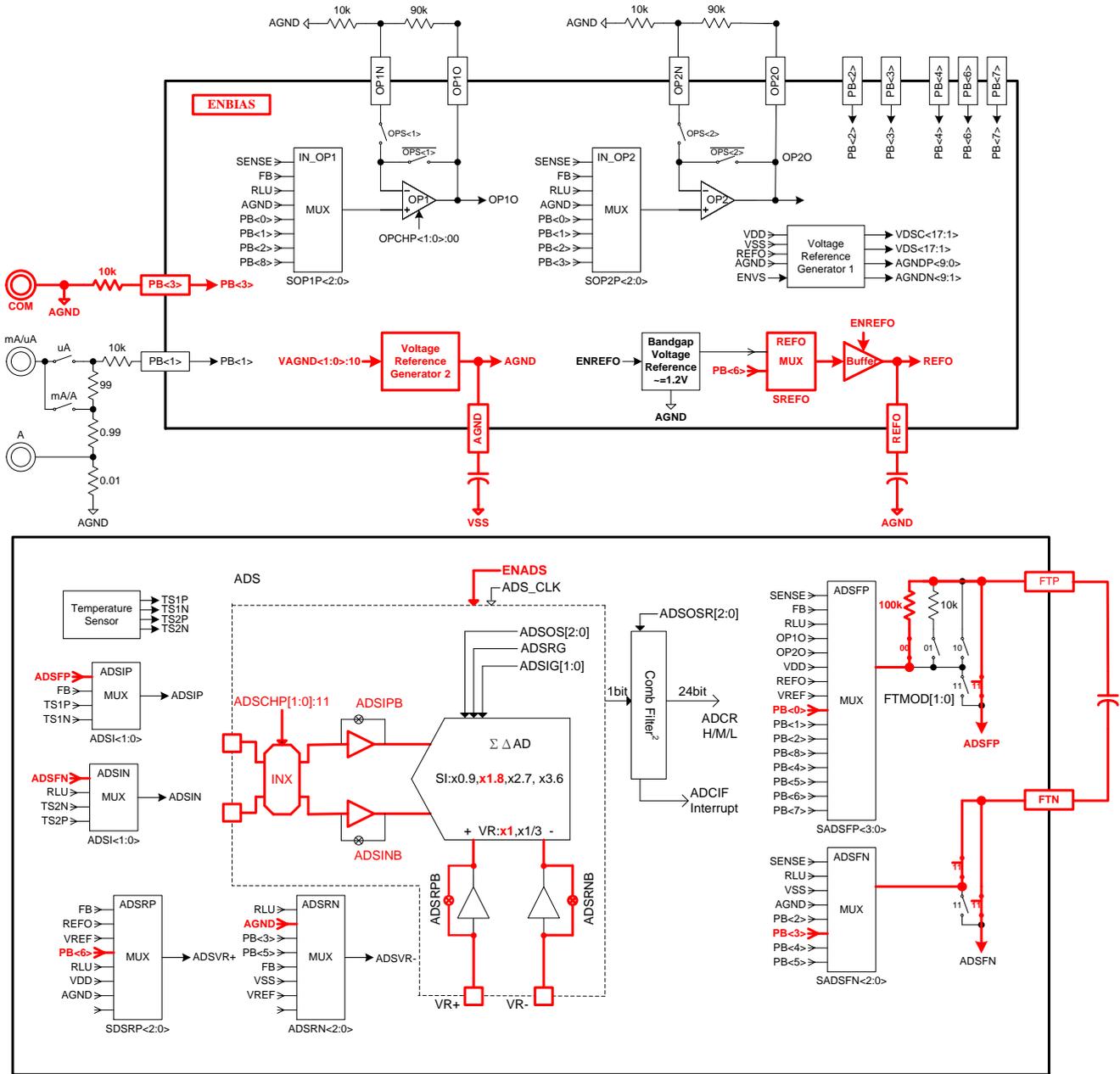7.2. Diode Measurement Network Configuration




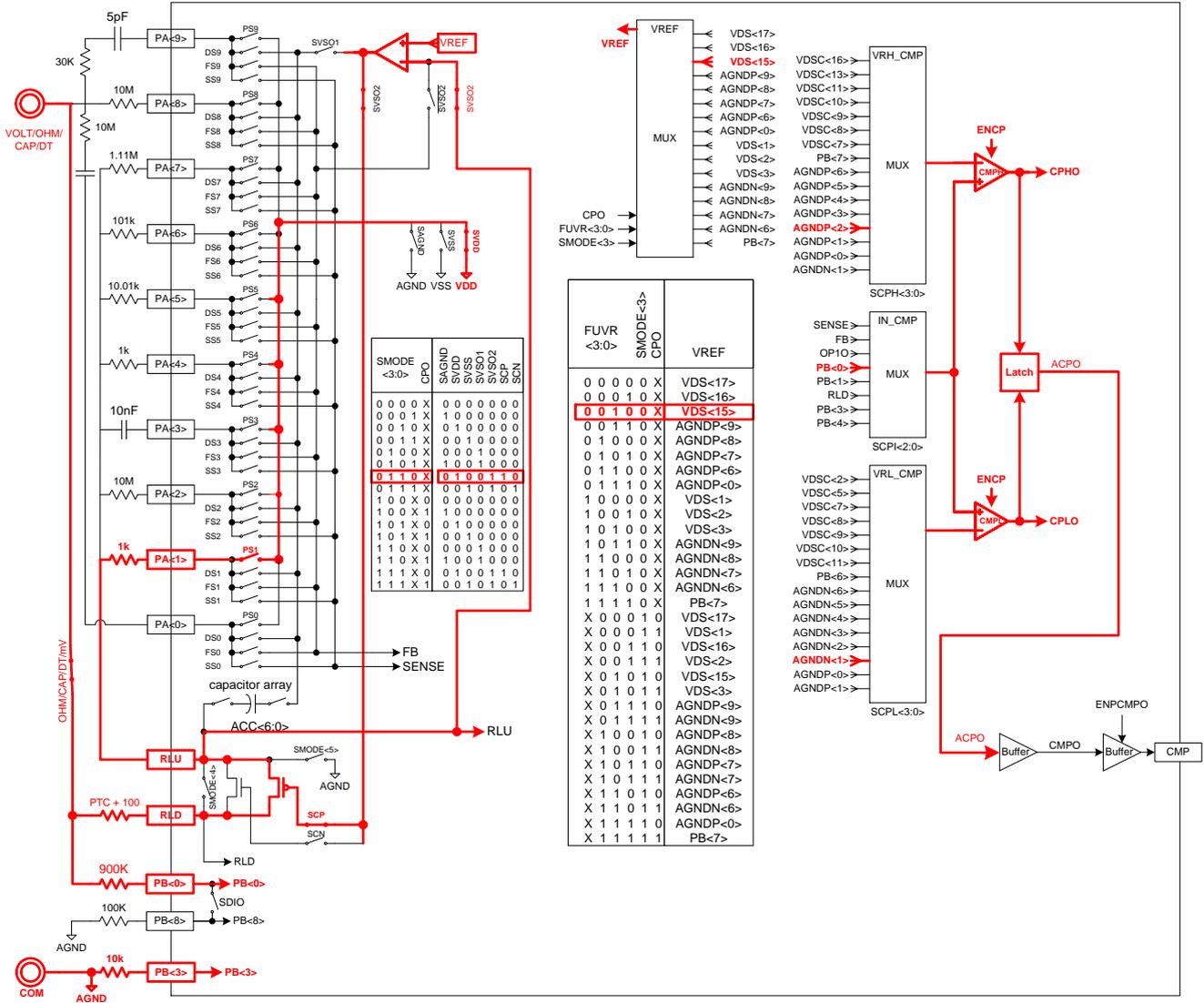8. Continuity


This function can use constant current or constant voltage output measurements. This case is positive constant current output measurement.



9.3. AC 50mA

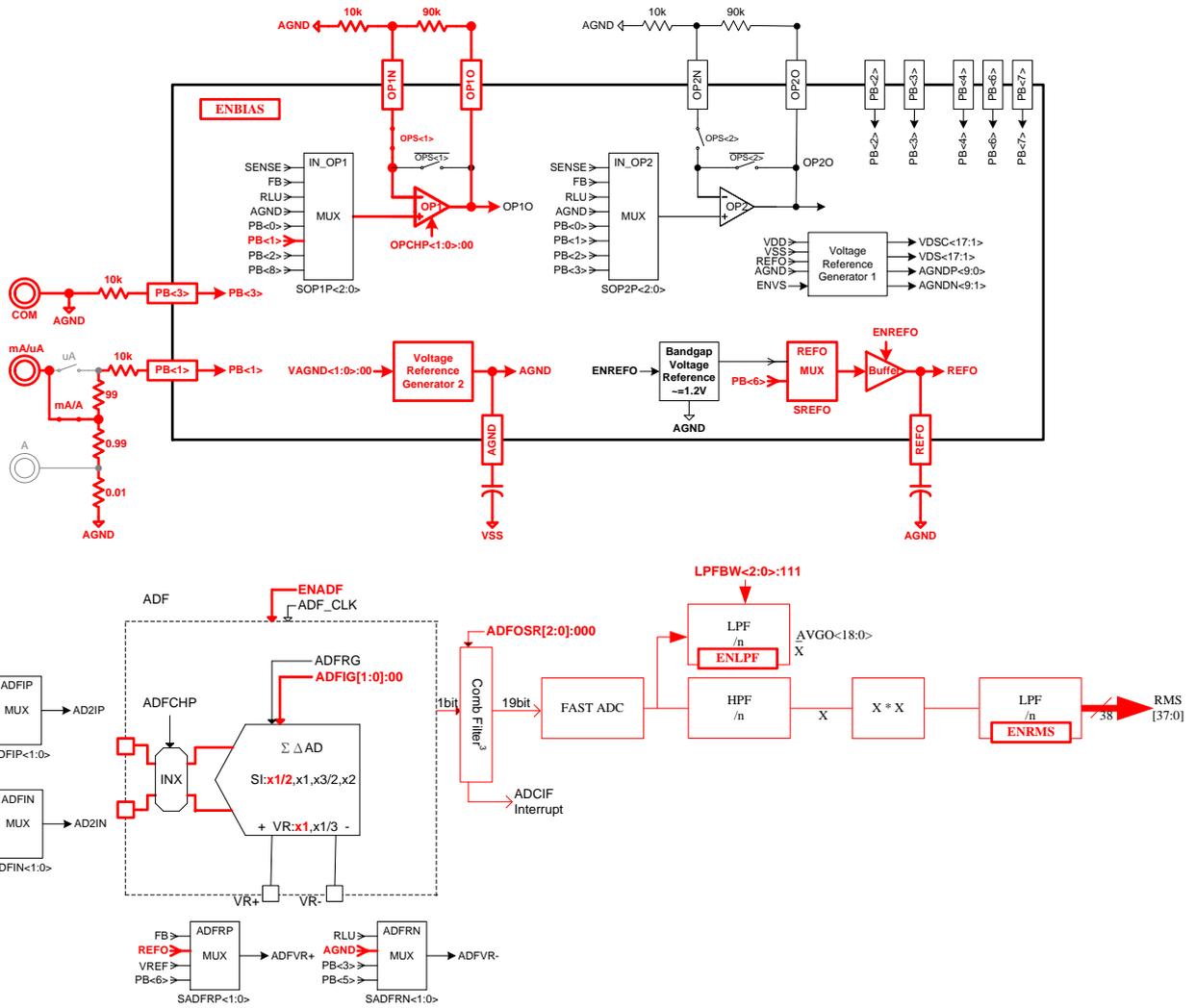


9.4. AC 500mA

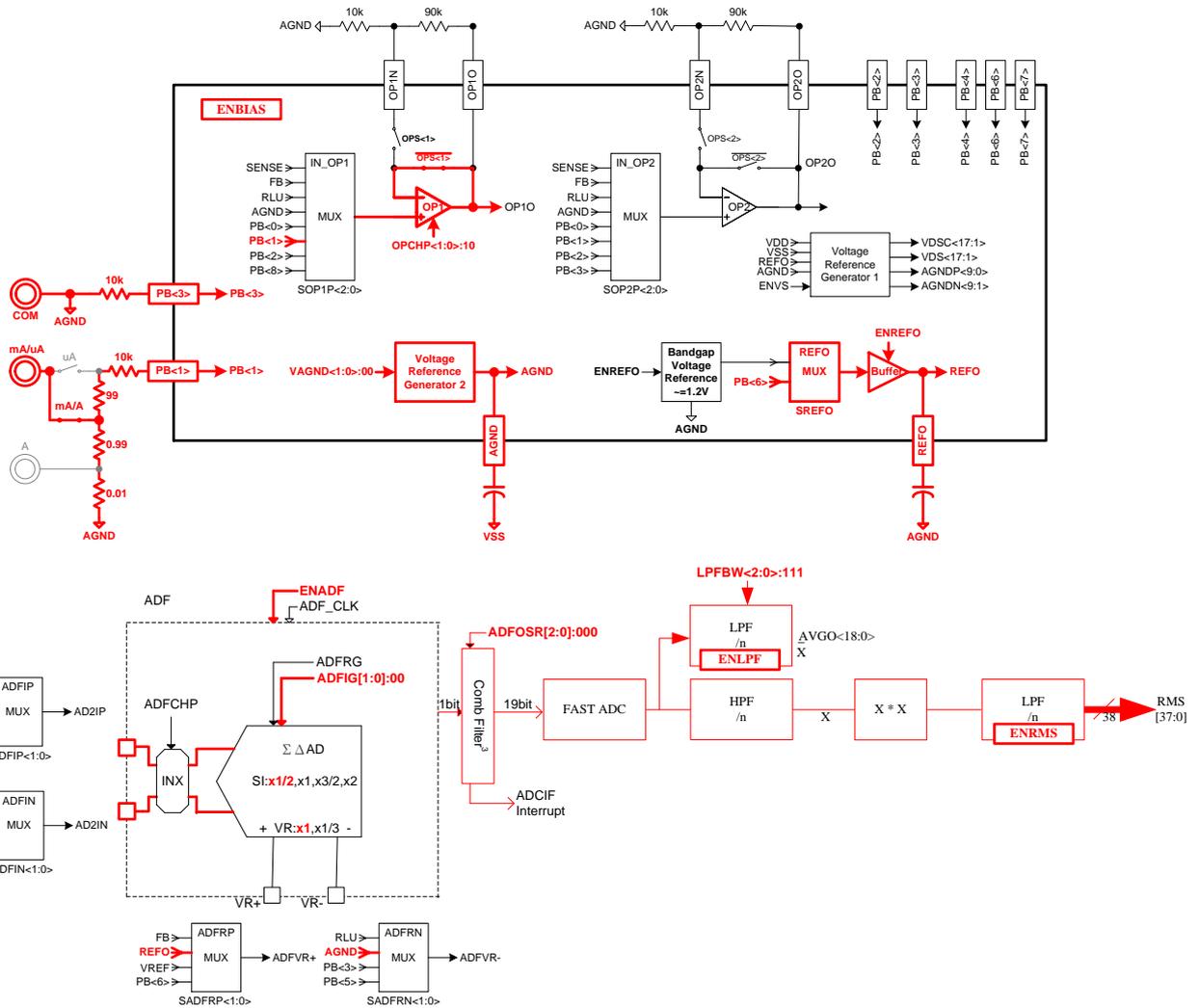


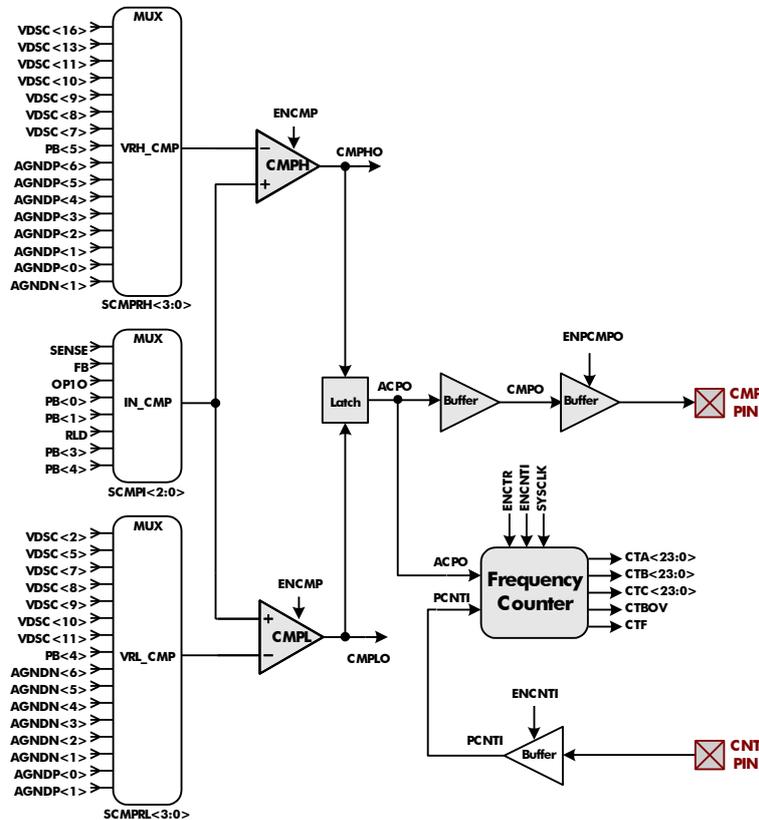10. Frequency


The frequency measurement can be divided into an analog input and a digital input. The analog input refers to the window comparator by PB<x> or PA<x>, and the comparator output (CMPO) is input to the Frequency Counter; the digital input is entered by the CNT to the Frequency Counter.



The analog input is only suitable for signal measurement with positive and negative half cycles. The positive trigger point of the window comparator is VRHCMP; the negative trigger point is VRLCMP. When the analog input signal reaches the positive trigger point of the window comparator, COMP is High; when the signal reaches the negative trigger point of the window comparator, COMP is Low. The comparator output (CMPO) function can be turned on during development of the product for easy debugging.

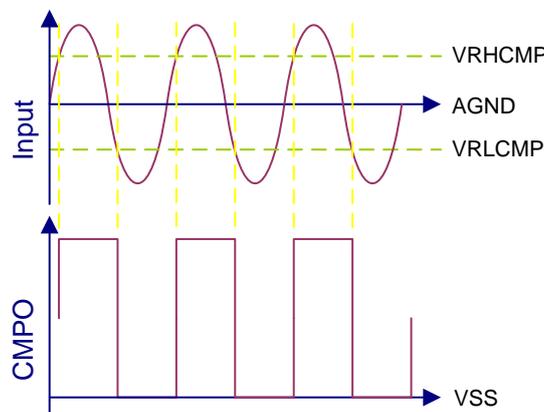

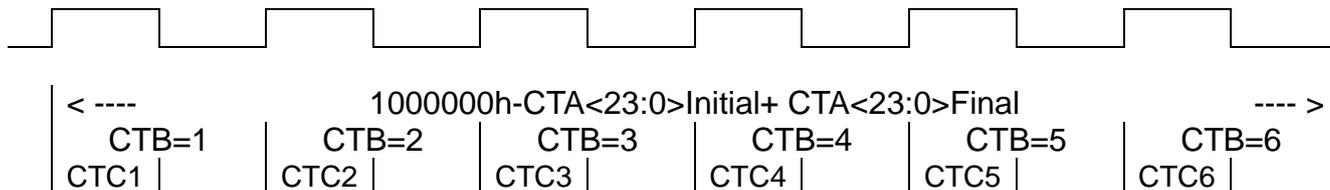10.1. Frequency Counter Calculation Example Description



Calculation condition description (1kHz / 50% as an example)

FSYSCLK: System oscillator frequency, assumed to be 4MHz

CTA<23:0>Initial: Preset value before CTA count, CTA<23:8> program defaults to C000h, and CTA<7:0> is cleared to 00h

CTA<23:0>Final: The value after the CTA is counted, CTA<23:0>Initial is C00000h, and in the case of 1kHz is 000760h

CTB<23:0>: Number of cycles in time, CTA<23:0>Initial is C00000h, and in the case of 1kHz is 000419h

CTC<23:0>: The sum of the time sum of High, CTA<23:0>Initial is C00000h, and at Duty 50% is 20043Ah

Count time:

$$T = [1000000h-CTA<23:0>Initial+ CTA<23:0>Final]/FSYSCLK$$

$$= (1000000h-C00000h +000760h)/3D0900h \text{ --- } > \text{hexadecimal}$$

$$= (16777216-12582912+1888)/4000000=1.0490 \text{ --- } > \text{decimal}$$

Standby signals frequency:

$$\text{Freq} = CTB<23:0>/T$$

$$= 1049/1.0490=1000 \text{ Hz}$$

Standby signal, Duty Cycle:


$$\text{Duty Cycle} = CTC<23:0>/[1000000h-CTA<23:0>Initial + CTA<23:0>Final]$$

$$= 20043Ah/400760h \text{ --- } > \text{hexadecimal}$$

$$= 2098234/4196192=0.5=50\% \text{ --- } > \text{decimal}$$

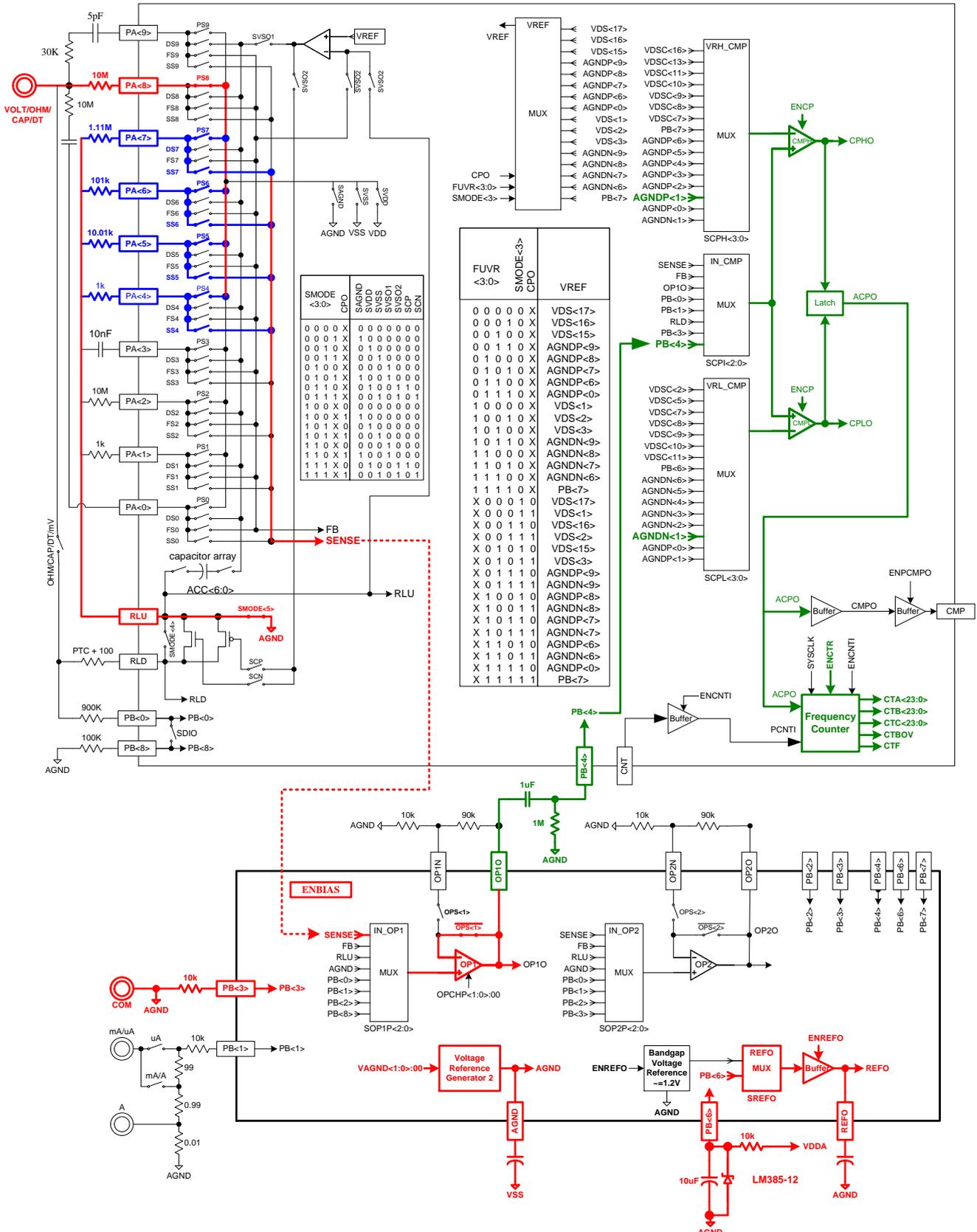
10.2. Voltage input (Analog Input)

When measured frequency, the signal is inputted by PA<n> and PB<n>. If the input contains DC, must be removed by AC Coupled capacitors.




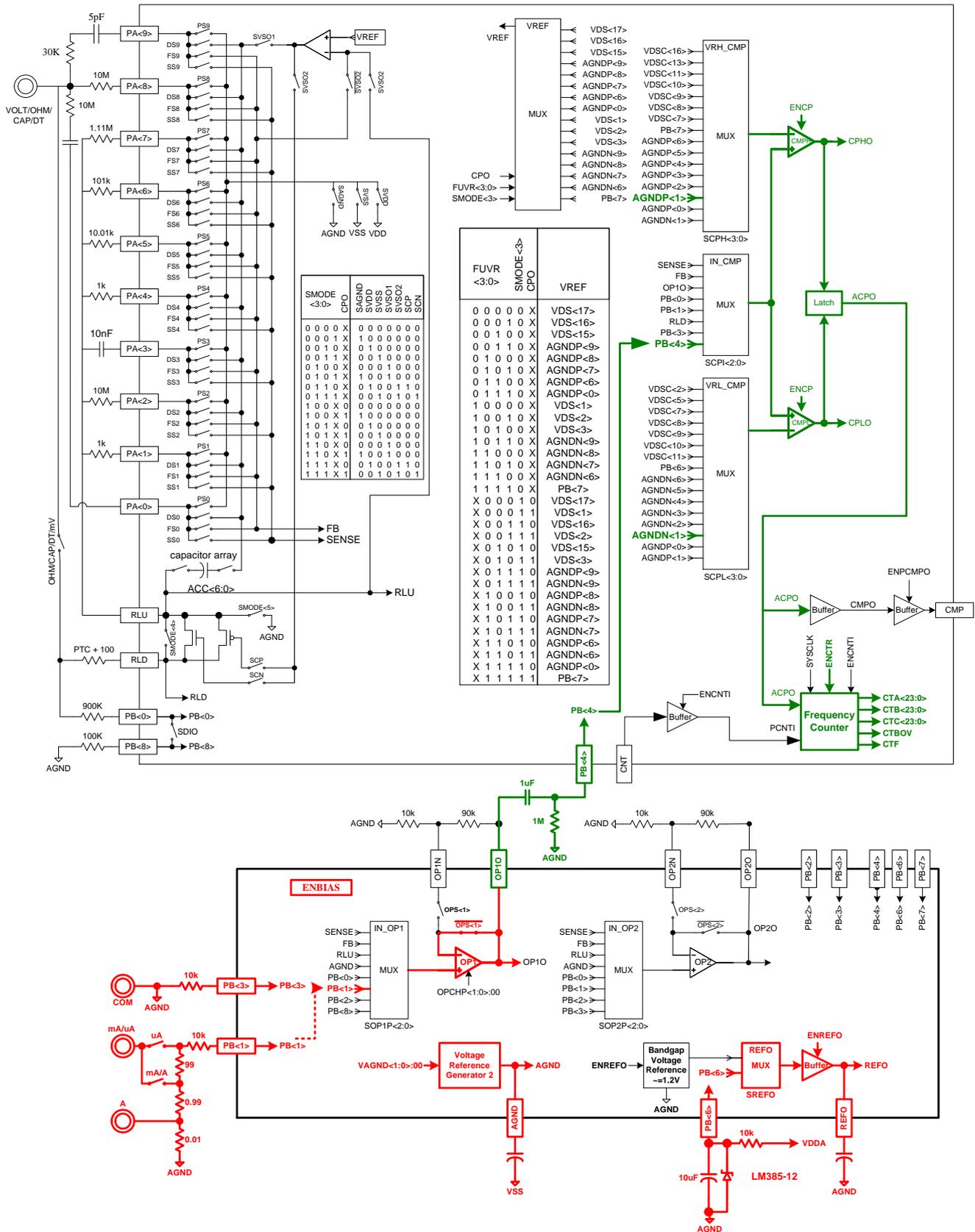10.3. Current input (Analog Input)

The current and measurement frequency method is entered into the window comparator by PB<1>, and the comparator output (CMPO) is input to the Frequency Counter.



10.4. CNT input (Digital Input)

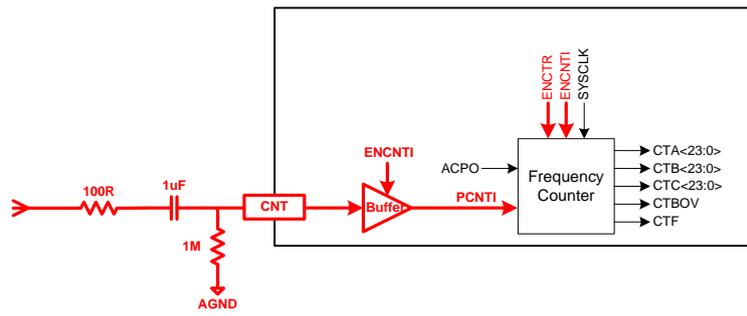

11. Revision History

Major differences are stated thereafter:

Version	Page	Revision Summary
V01	All	First edition
V02	All	Revise all contents
V04	17	Explain how the capacitance value is calculated all contents
	23	Revise SMODE setting for constant voltage and constant current test mode out.
	29	Added charging and discharging descriptions and figure
	49~53	Added Chapter 10 Frequency Description
V05	All	Modify the external resistance value & capacitance value to match the calculated value (From 1M→1.11M, from 100K→101K, from 10K→10.01K 100nF→10nF)